
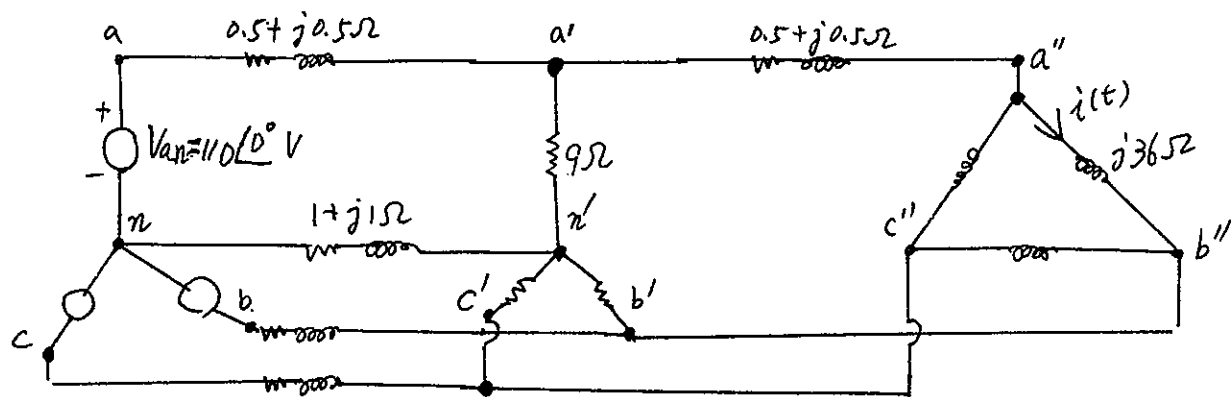


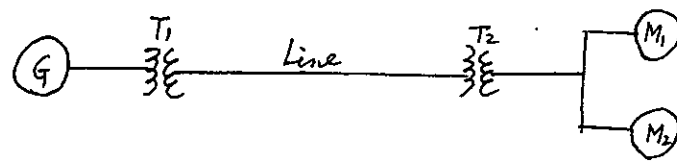
- Given a salient-pole synchronous generator with terminal voltage $V_a = 1.0 \angle 0^\circ$, $X_d = 1.0$, $X_q = 0.6$ (d- and q- axis synchronous reactance), r (armature resistance) = 0.005. Find the open-circuit voltage when the armature current is $I_a = 0.8 \angle -60^\circ$. (15%)
- Given the 60 Hz, balanced three-phase system shown below, find $i(t)$. (15%)



- A three-phase, 10 HP, four-pole Y-connected three-phase induction motor is supplied power from a balanced three-phase 60 Hz source of 220 V line-to-line. Determine the frequency of the rotor current when it is rotating at a speed of 1000r/min. (12%)
- Draw an impedance diagram and compute the per-unit impedances for the system whose one-line diagram is shown below. The three phase and line-line ratings are as follows:
 - Generator G : 20 MVA, 13.8 KV, $X = 0.1$ p.u.
 - Motor M1 : 5MVA, 14.4 KV, $X = 0.15$ p.u.
 - Motor M2 : 10 MVA, 14.4 KV, $X = 0.15$ p.u.
 - Transformer T1: 30 MVA, 13.2-161 KV, $X = 0.1$ p.u.
 - Transformer T2: 20 MVA, 161-13.8 KV, $X = 0.1$ p.u.
 - Line : $20 + j120$ ohm (actual)
 Select a base of 30 MVA and 161 KV in the transmission line. (12%)




- Let $|V_1| = 1.05$, $|V_2| = 1$, $Z_{line} = 0.6 \angle 80^\circ$, $\theta_{12} = \theta_1 - \theta_2$. For what nonzero θ_{12} is S_{12} purely reactive? ($0 < \theta_{12} < 2\pi$) (12%)

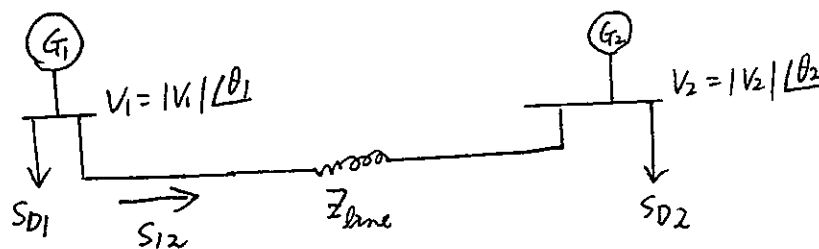

見背面

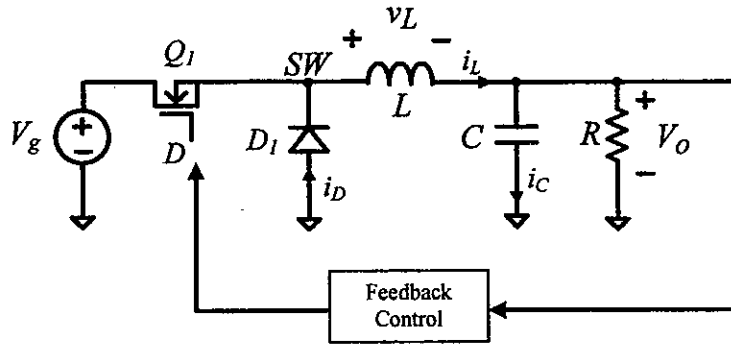
6. A buck converter below operates at steady-state and discontinuous conduction mode (DCM). Assume the converter is ideal.



- How many modes do the converter operates in DCM? Draw the equivalent circuit of each mode. (3%)
- Derive the input to output dc gain (V_g/V_o) as a function of circuit variables such as L , C , R and duty cycle D . (5%)
- Derive the criteria for the converter operates at DCM. (3%)
- Sketch the time waveforms of D , SW voltage, i_L , i_C . Mark peak and valley values (7%)

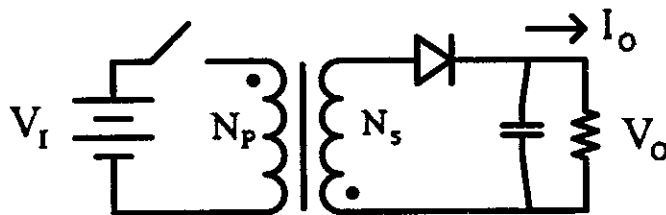7. Answer below questions. Explanation or mathematic derivations are required.

- What is the value of integration of capacitor current across a switching period at steady-state? (3%)?
- Why the diode D in the flyback converter below will turn-on after switch turn-off? (4%) (hint: Draw the equivalent circuit of Flyback converter)




- A buck-boost converter in CCM operation as below. Assume there is a small parasitic inductance in series with the switch. Draw the voltage waveform across this inductor and duty waveform for two switching periods. (5%)

接次頁

題號： 358
科目： 電力工程
節次： 8

國立臺灣大學 111 學年度碩士班招生考試試題

題號： 358
共 3 頁之第 3 頁

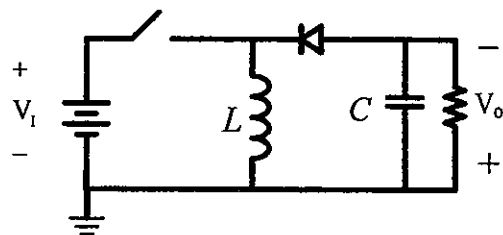

- (d) Draw the Bode plot (gain and phase plots) of the transfer function $T = \frac{10}{s(s+10)}$
(4%)

試題隨卷繳回