

- For the circuit shown in Fig. 1, please use **Nodal analysis** to determine: (a) the node voltage V_1 and V_2 , and (b) the power **supplied** by the dependent current source $\langle 3i_1 \rangle$. [20]
- For the circuit shown in Fig. 2, the supply voltages of the op-amp are: $+V_{CC} = 15V$ and $-V_{CC} = -15V$. The values of the resistors are: $R_1 = 2k\Omega$, $R_2 = 1k\Omega$, $R_3 = 1k\Omega$, $R_4 = 2k\Omega$. The input voltages are $v_1 = 1.5V$ and $v_2 = 2V$. (a) Please determine the output voltage v_o . (b) if the resistors are changed to $R_1 = 1k\Omega$, $R_2 = 0.5k\Omega$, $R_3 = 1k\Omega$, $R_4 = 14k\Omega$ and the input voltages remains the same, please determine the output voltage v_o . [15]
- The circuit shown in Fig. 3 has $L = 200\mu H$, $C = 27\mu C$, and $R = 5\Omega$. The time-domain differential equation can be derived as (1) and the frequency-domain equation can be derived as (2).

$$X \cdot \frac{d^2 v_c}{dt^2} + Y \cdot \frac{dv_c}{dt} + Z \cdot v_c = K \quad \dots\dots (1)$$

$$U \cdot s^2 v_c(s) + V \cdot s v_c(s) + W \cdot v_c(s) = J \quad \dots\dots (2).$$
 Please answer the following questions: (a) Determine the values for X, Y, Z, K, U, V, W, and J. [15]; (b) Determine the frequency-domain transfer function $H(s) = v_o(s)/v_i(s)$. [5]; (c) Draw the Bode plot (both magnitude and phase) of $H(s)$. [10] (d) If the input voltage is $v_i(t) = 110 \sin(377t)$ V, what is the out voltage $v_o(t) = ?$ [5] (e) If the input voltage is $v_i(t) = 110 \sin(13600t)$ V, what is the out voltage $v_o(t) = ?$ [5]
- For the circuit shown in Fig. 4 the input current $i_{in} = 3A$ for $t < 0$ and $i_{in} = -1A$ for $t \geq 0$. (a) Please determine the s-domain expression of inductor current $I_L(s)$. (b) Determine the time-domain inductor current $i_L(t)$. [20]
- Please explain the principle of superposition. [5]

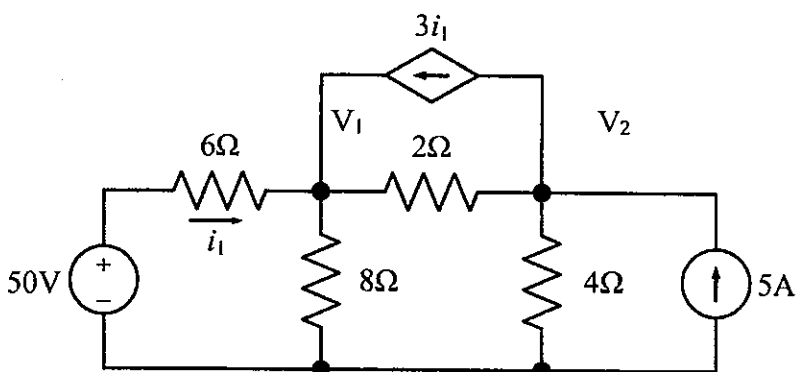


Fig. 1

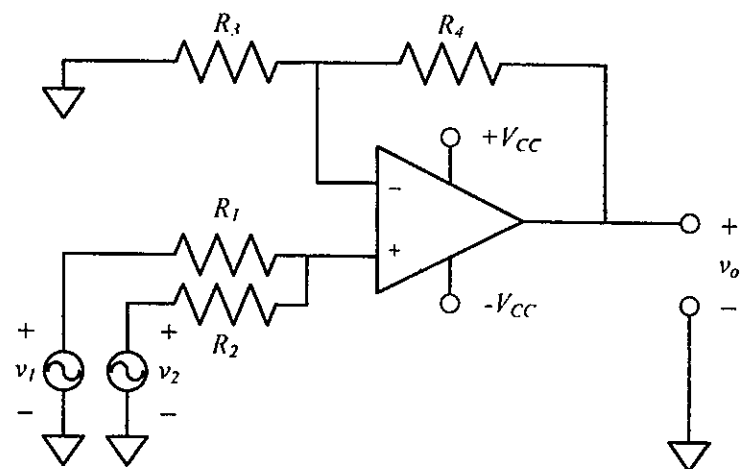


Fig. 2

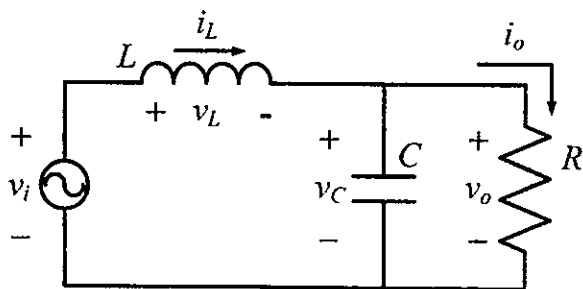


Fig. 3

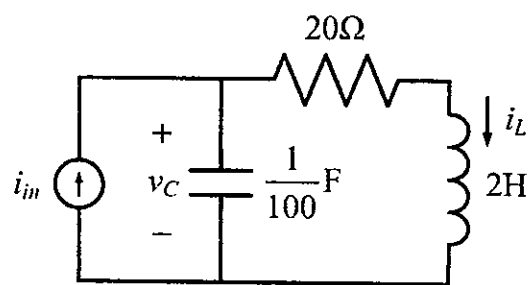


Fig. 4