
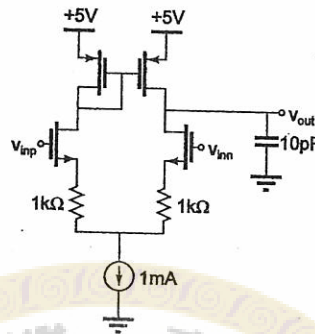


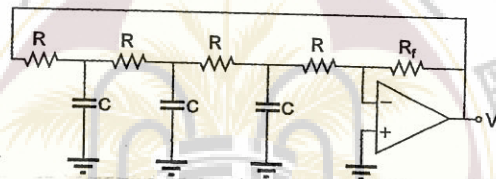
1. (30 分) Please find the unity-gain bandwidth for the following amplifier. [$\mu_n C_{ox} = 100 \mu A/V^2$, $\mu_p C_{ox} = 50 \mu A/V^2$, $V_{in} = -V_{tp} = 0.5V$, and $\lambda = 0.05V^{-1}$. Please assume all transistors are biased correctly in the saturation region and all have ratios of 10/1.]



2. (25 分) Assume $C = 1nF$, please find R and R_f such that an oscillation of 100kHz can be obtained.



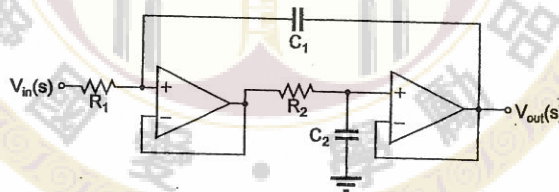3. (30 分) The following circuit is a second-order low-pass filter. (a) Please find the transfer function $[V_{out}(s)/V_{in}(s)]$ in terms of R_1 , R_2 , C_1 , C_2 , and s . (b) Assume $C_1 = C_2 = 100pF$, please find R_1 and R_2 such that the filter is a second-order butterworth low-pass filter with a 3-dB cutoff frequency of 1MHz.



4. (15 分) Please draw the CMOS realization of $(A(B+CD))'$ without cascading logic gates and with only A, B, C, and D as inputs.

試題隨卷繳回