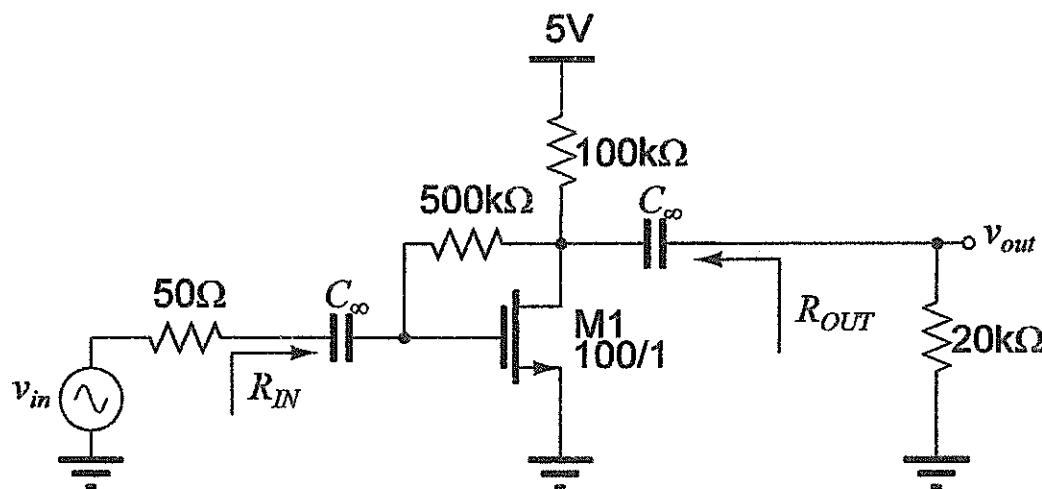


- For the following amplifier circuit, please find
 - (20%) the dc operating point of the transistor (I_{DS} & V_{GS} , neglect λ for dc),
 - (10%) the small-signal gain (v_{OUT}/v_{IN}),
 - (10%) the input resistance R_{IN} ,
 - (10%) the output resistance R_{OUT} ,
 - (10%) the quiescent power dissipation P_{diss} .


[note: $\mu_n C_{ox} = 120 \mu\text{A/V}^2$, $V_{tn} = 0.7 \text{ V}$, and $\lambda_n = 0.04 \text{ V}^{-1}$]



2. For the lower-left source-degenerated differential amplifier, all transistors have W/L of 100/1, $\mu_n C_{ox} = 120 \mu\text{A/V}^2$, $V_{tn} = 0.7 \text{ V}$, and $\lambda_n = 0.04 \text{ V}^{-1}$. Please find

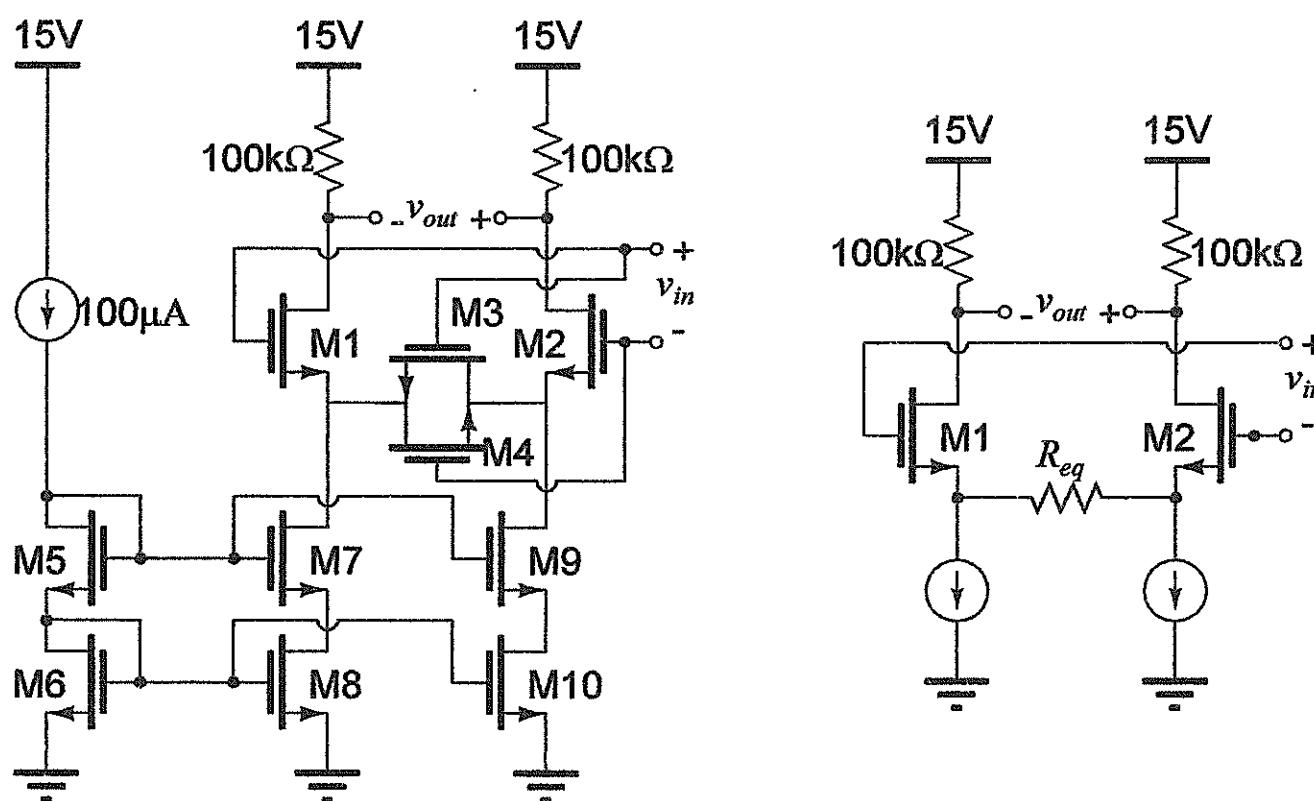 - (a) (10%) the equivalent resistance R_{eq} of M3 and M4 in parallel (hint: M3&M4 are in the triode region),
 - (b) (10%) the differential small-signal gain ($A_d = v_{od}/v_{id}$) if M1,M2,M5~M10 are in the saturation region,
 - (c) (10%) the quiescent power dissipation P_{diss} ,
 - (d) (10%) the input common-mode range (ICMR).

(Hint: the lower-right circuit is the equivalent circuit of the lower-left one)



試題隨卷繳回