

- For the circuits shown in Fig. 1, assuming that the opamps are ideal.
 - For Fig. 1(a), derive an expression for the differential voltage gain, V_{out}/V_{in} . (10%)
 - In Fig. 1(b), let $C_2 = C_4 = C$, $C_1 = 10C$, $C_3 = 8C$, and $R_l = R$, please derive an expression for the differential voltage gain, V_{out}/V_{in} . (10%)
 - Plot the frequency response of the voltage gain (V_{out}/V_{in}) derived in (b). You must denote key parameters in the plot. (10%)

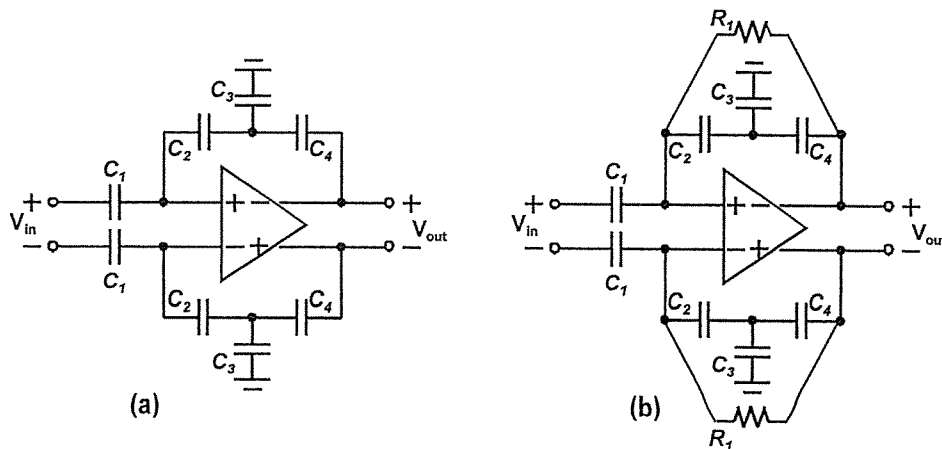


Fig. 1

- Please refer to Fig. 2.
 - For the circuit of Fig. 2(a), it consists of 2 trans-conductors and a capacitor. Please derive an expression for its input impedance, Z_{in} . What is the purpose of this circuit? (10%)
 - For the circuit of Fig. 2(b), assuming V_b , I_1 , and I_2 are chosen appropriately such that this circuit is properly biased. Considering transistor parasitic capacitance, but ignoring the channel-length modulation effect, please derive an expression for the input impedance, Z_{in} . (10%)
 - Next, derive an expression for the input impedance, Z_{in} , when channel-length modulation effect is considered. How does this affect the circuit performance? (10%)

 


Fig. 2

見背面

3. Fig. 3 depicts an SRAM cell.

- Describe the **Read** operation of the SRAM cell. Please draw related timing waveforms to assist your description. (5%)
- Describe the **Write** operation of the SRAM cell. Please draw related timing waveforms to assist your description. (5%)
- How are the sizes of access transistors (Q_5/Q_6), NMOS transistors (Q_1/Q_3), and PMOS transistors (Q_2/Q_4) determined? Please discuss the design guidelines. (10%)

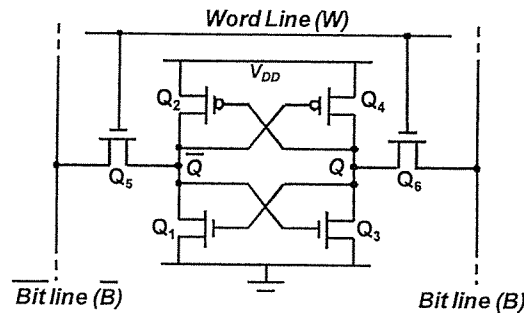


Fig. 3

4. Fig. 4 depicts an amplifier circuit.

- Derive expressions for the voltage gain, $V_{out}/(V_2 - V_1)$, and the output resistance, R_{out} . (10%)
- This circuit has the following parameters: $I_{bias} = 0.2$ mA, $V_{DD} = 3$ V, $R_I = 2$ k Ω ; NMOS parameters are: $K_n = 4$ mA/V², $V_{TN} = 1$ V, $V_A = 40$ V; PMOS parameters are: $K_p = 1$ mA/V², $V_{TP} = -1$ V, $V_A = 25$ V. Calculate the voltage gain and output resistance derived in (a). (5%)
- What may be the purpose of adding two resistors (the two R_I) to this circuit? What are the penalties by doing so? (5%)

 


Fig. 4

試題隨卷繳回