

1. In Fig. 1, let the op amp be ideal:

- (a) Please derive the transfer function (7%).
- (b) Please sketch a Bode plot for the magnitude response (10%).

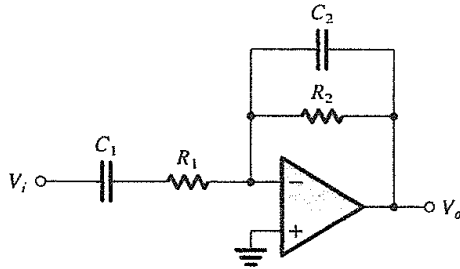


Fig. 1

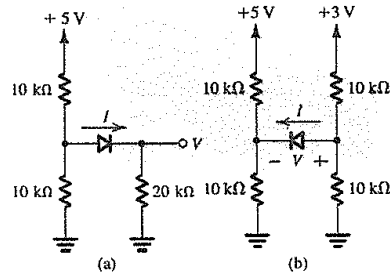


Fig. 2

- 2. Assuming that the diodes in the circuits of Fig. 2 are ideal, please find the values of the labeled currents and voltages (8%).
- 3. Consider the amplifier circuit shown in Fig. 3. The BJT has $|V_{BE}| = 0.7 \text{ V}$, $\beta = 200$, $C_{\mu} = 0.8 \text{ pF}$, and $f_T = 600 \text{ MHz}$. The MOSFET has $V_t = 1 \text{ V}$, $k'W/L = 2 \text{ mA/V}^2$, and $C_{gs} = C_{gd} = 1 \text{ pF}$.
 - (a) Please determine the amplifier input resistance R_{in} , and the overall voltage gain V_o/V_{sig} . Assume r_o of both transistors to be very large (12%).
 - (b) Consider the circuit at low frequencies. Please find the frequency of the poles due to C_1 and C_2 , and hence estimate the lower 3-dB frequency, f_L (10%).
 - (c) Consider the circuit at higher frequencies. Please use open-circuit time constants to estimate f_H (8%).

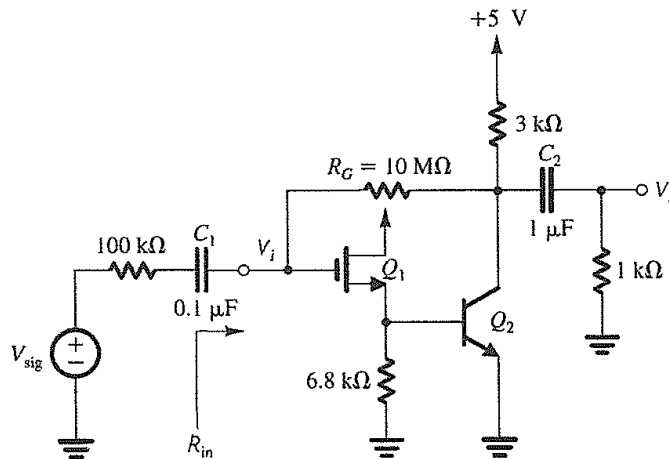


Fig. 3

- 4. For the current-mirror-loaded differential amplifier in Fig. 4. Assume $\beta = 100$, $|V_{BE}| = 0.7 \text{ V}$, $|V_A| = 60 \text{ V}$, $V_t = 0.7 \text{ V}$, and $k'(W/L) = 2 \text{ mA/V}^2$. Please find: (a) differential input resistance (R_{id}) (5%), (b) A_d (5%), and (c) CMRR (5%).

見背面

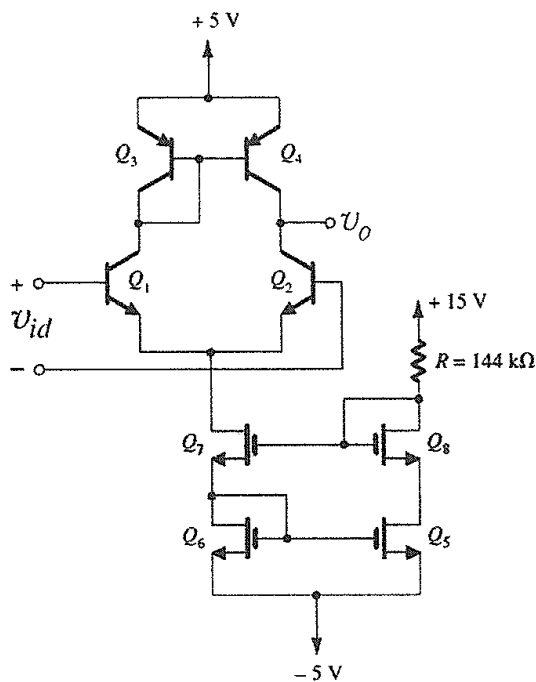


Fig. 4

5. The capacitors of Fig. 5 are uncharged. The switch is closed at $t = 0$ s for 8 ms. (a) Please determine v_c and i_c during charge (4%). (b) Through the charging process, are the capacitors in steady state? Please explain it 4%. (c) Please find the magnitude of the charge and energy stored on the 10- and 40- μ F capacitors at $t = 8$ ms, respectively (4%). After 8 ms, the switch is opened. (d) Please find v_c and i_c during discharge (4%). (e) Please estimate how long will the transient last. (4%)

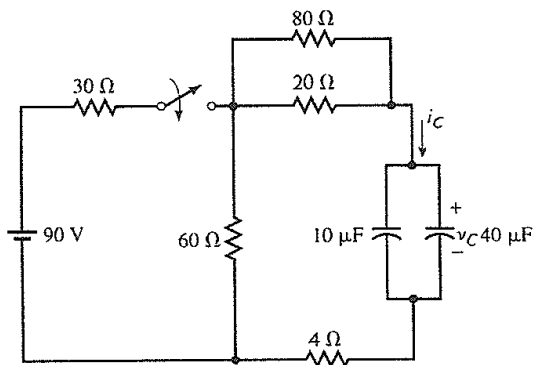


Fig. 5

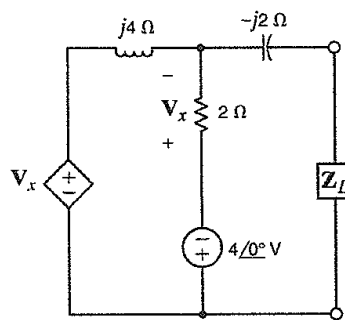


Fig. 6

6. In Fig. 6, please find Z_L for maximum average power transfer and please compute the maximum average power supplied to the load. (10%)

試題隨卷繳回