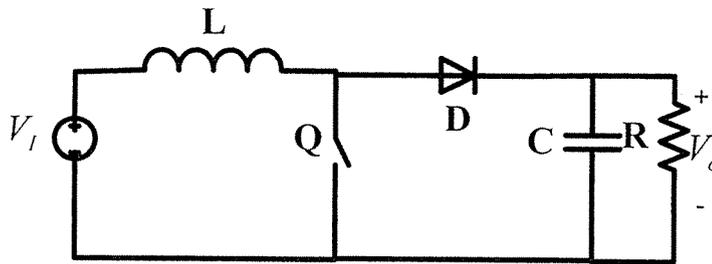


1.



$V_i = 10\text{V}$, Q duty cycle = 50%, $L = 200\mu\text{H}$, C : large
 $R = 2\Omega$, $f_s = 100\text{kHz}$, all ideal semiconductor components.

- (a) Under this condition, is the converter operating in a Continuous Conduction Mode (CCM) or Discontinuous Conduction Mode (DCM)? (8%)
- (b) Sketch $i_c(t)$ waveform (Just the wave shape. No need to indicate the amplitude.) (5%)
- (c) What's the input average current? $(I_{in})_{avg}$ (5%)

見背面


3. 有一台單相理想變壓器，頻率 f 為 60 Hz ，一次側電壓 V_1 為 2000 伏特，一次側電流 I_1 為 5 A ，一次側匝數 N_1 為 200 匝，二次側匝數為 40 匝，試求此變壓器下列問題：

- (1) 二次側電壓 V_2 為若干伏特 (V)。 (5%)
- (2) 二次側電流 I_2 為若干安培 (A)。 (5%)
- (3) 容量為若干仟伏安 (kVA)。 (3%)

4. 有一 12 極， 60 Hz 三相同步電動機，具同步電抗為 $6\ \Omega/\text{相}$ ，激磁電壓 $E_f = 3500$ 伏特/相，端電壓 $V_t = 3800$ 伏特/相，求功率角 $\delta = 30^\circ$ 時之


- (1) 輸出功率 (kW)。 (10%)
- (2) 輸出轉矩 (牛頓-米)。 (10%)

見背面

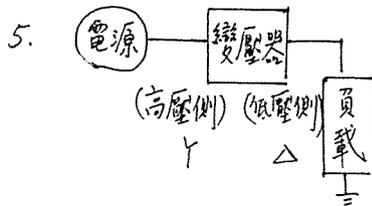


左圖所示為一三相電源經由一三相變壓器供電給三相負載。此三相變壓器是由三台單相變壓器所組成，每台單相變壓器之額定值為 12 KV/220V, 2MVA, 漏電抗 $X_l = 0.12 \text{ pu}$ 。變壓器之電阻及激磁電流可忽略不計。

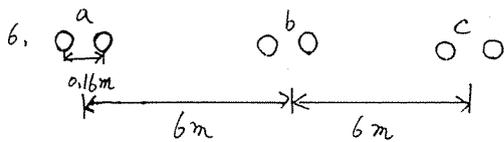- (a) 若選定高壓側之基準值為 22KV, 8MVA, 試求三相變壓器漏電抗之標么值。(7%)
- (b) 當三相負載之有效電力為 3.6 MW, 負載功因為 0.85 落後時, 試求電源側電壓之標么值。(假設負載端之線電壓為 225V) (7%)



左圖所示為一 60Hz 三相平衡且完全换位 (COMPLETELY TRANSPOSED) 之輸電線,

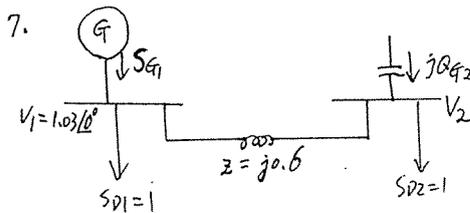每根導線之半徑為 1.6 cm。此輸電線之磁通鏈為 $\begin{bmatrix} \lambda_a \\ \lambda_b \\ \lambda_c \end{bmatrix} = L_{abc} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix}$, 而其電荷為 $\begin{bmatrix} q_a \\ q_b \\ q_c \end{bmatrix} = C_{abc} \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix}$, 試求矩陣 L_{abc} 及 C_{abc} 。(10%)



當 $|V_2| = 1$ 時, 試求 Q_{f2} 。(10%)