
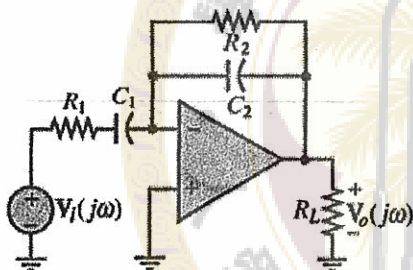


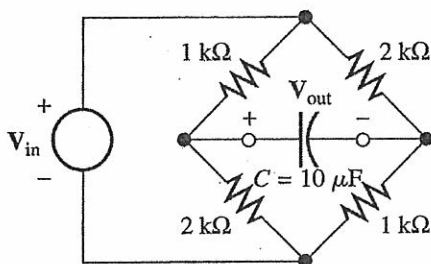1. Please draw the electron concentration versus temperature (temperature from 0K to 1000K) for an n-type semiconduction doped at $1 \times 10^{14} \text{ cm}^{-3}$.
 - a) Please indicate the three regions in the plot. (6%)
 - b) Please draw the energy diagram of each region. (6%)
 - c) Please use a) and b) to explain the curve trend of each region. (6%)
2. The reverse saturation current densities in a pn junction diode and a Shottky diode are $5 \times 10^{-12} \text{ A/cm}^2$ and $7 \times 10^{-8} \text{ A/cm}^2$, respectively, at $T=300\text{K}$. The cross-sectional area of the pn junction diode is $A=8 \times 10^{-4} \text{ cm}^2$. Determine the cross-sectional area of the Shottky diode so that the difference in forward-bias voltages to achieve 1.2 mA is 0.265V. (7%)
3. Analyze the basic OP Amp circuit in the following figure: $C_2=C_1=0.1\mu\text{F}$, $R_1=R_2=10\text{K}\Omega$.
 - a) The gain or transfer function of this filter. (5%)
 - b) The resonant frequency of this filter. (5%)
 - c) The cutoff frequency (frequencies) of this filter. (5%)
 - d) The circuit Q. (5%)
 - e) Sketch the Bode Plot. Is this circuit a low-pass, band-pass or high-pass filter? (5%)



4. A multipole amplifier having the first pole at 8 MHz and a dc open-loop gain of 60 dB is to be compensated for closed-loop gains as low as unity by the introduction of a new dominant pole. At what frequency must the new pole be placed? (15%)
5. Find the transfer function of the following circuit and determine the value of the half-power frequency. (15%)




6. (a) For the following folded-cascode CMOS op amp, please indicate clearly the plus (+) and minus (-) signs for the inputs (V_{in1} and V_{in2}) and explain why the input polarity is correct for your assignment. (10%)
 - (b) Please find the output resistance of the op amp. (10%)

見背面

題號： 422
科目：電子學(E)
節次： 4

國立臺灣大學101學年度碩士班招生考試試題

題號： 422
共 2 頁之第 2 頁

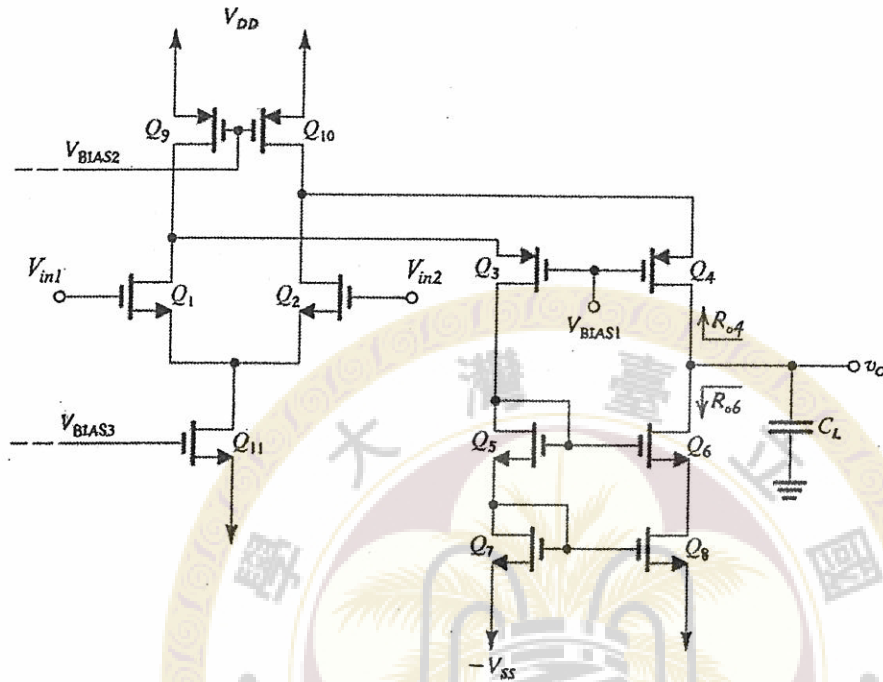

試題隨卷繳回