
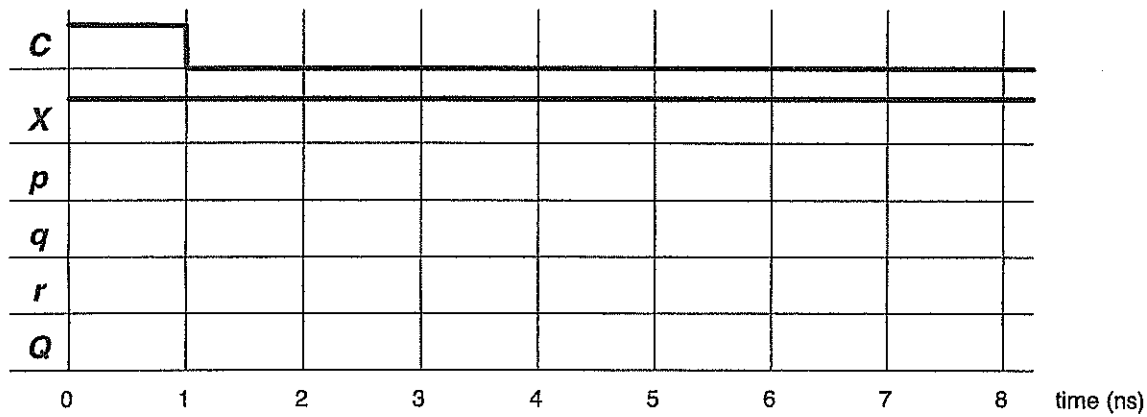


Problem 1 (25%)

Consider the gated X-latch below where X is the input and C the gate input.

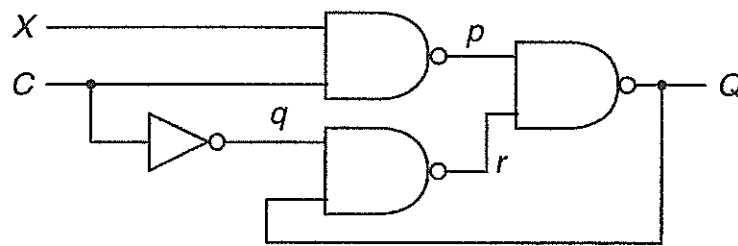- (a) What's the next-state equation of the X-latch? (5%)
- (b) Assume that each gate has a 1 ns delay. Complete the timing diagram below. (10%)
- (c) Does the X-latch works correctly? If not, fix the problem and justify your solution. (10%)




Problem 2 (20%)

Derive a minimal state table for a single-input and single-output Moore-type FSM that produces an output of 1 if in the input sequence it detects either 110 or 101 patterns. Overlapping sequences should be detected.

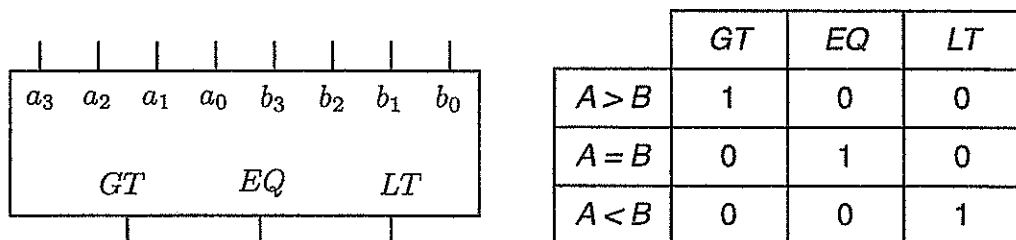Problem 3 (15%)

The 4-bit comparator below compares two binary numbers $A = a_3a_2a_1a_0$ and $B = b_3b_2b_1b_0$ and produces greater than (GT), equal (EQ), and less than (LT) outputs according to the table below. Show how to construct an 8-bit comparator with two 4-bit ones and external logic.




見背面

Problem 4 (10%)

Implement the following functions using only two of the decoders described below and two 8-input OR gates.

$$f(w, x, y, z) = \sum m(0,4,5,7,8,12,15)$$
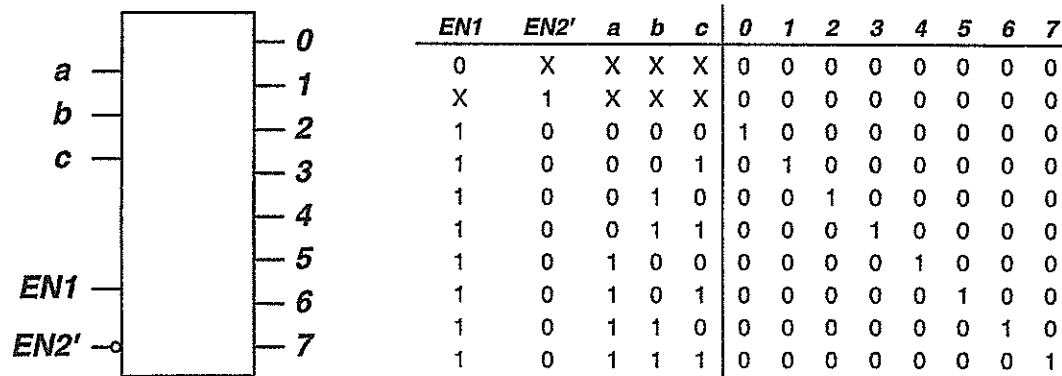
$$g(w, x, y, z) = \sum m(1,3,5,12,13,14)$$



Problem 5 (15%)


Find "all" minimum sum of products expressions for f and g .

$$f(a, b, c, d) = \sum m(0,2,3,5,7,8,9,10,11) + \sum d(4,15)$$

$$g(a, b, c, d) = \sum m(0,2,4,5,6,7,8,9,10,14) + \sum d(3,13)$$

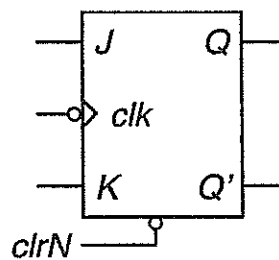Problem 6 (15%)

Construct a base 20 "asynchronous" counter that counts the number of input pulses (from 0 to 19, back to 0, and repeat) using JK flip flops, which, as shown below, are falling-edge triggered and have an active-low clear input, $clrN$. Denote the counter output by $C = C_4C_3C_2C_1C_0$.



試題隨卷繳回