

- For the circuit shown in Fig. 1 with input voltage $V_1=2V$ and $V_2=6V$. (a) Please determine the output voltage $V_{out} = ?$ (b) If R_f is replaced by a $600\text{ k}\Omega$ resistor, what is the new output voltage $V_{out} = ?$ [20]
- For the circuit shown in Fig. 2, please use mesh analysis method to determine the current I_2 . [20]
- The switch S shown in Fig. 3 had been closed for a long time. It opens at $t = 0$. Please find the capacitor voltage $v_C(t)$ for $t > 0$. [20]
- The induction motor, IM, in Fig. 4 draws 10 KVA, 40 Arms, at power factor $PF=0.8$ lagging. Please determine the value of the capacitor C to allow the 220Vrms, 60Hz source to operate at power factor $PF=0.95$ lagging. [20]
- For the circuit shown in Fig. 5, the given input voltage is: $v_s(t) = 20\text{ V}$ for $t < 0$; $v_s(t) = -20\text{ V}$ for $t > 0$. Please (a) draw the s-domain equivalent circuit with input and initial-value sources [5]; (b) determine the s-domain expression of capacitor voltage $V_C(s)$ [5]; (c) determine the time-domain expression of $v_C(t)$ for $t > 0$. [10]

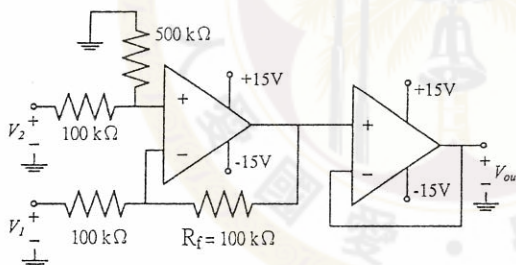


Fig. 1

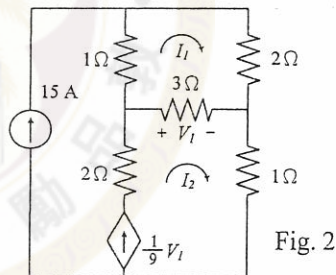


Fig. 2

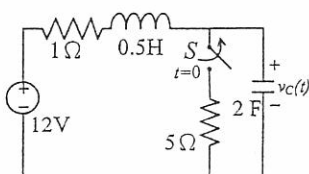


Fig. 3

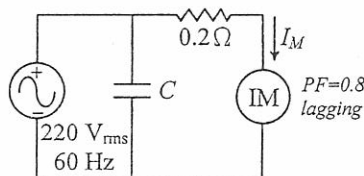


Fig. 4

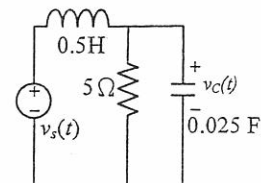


Fig. 5

試題隨卷繳回