
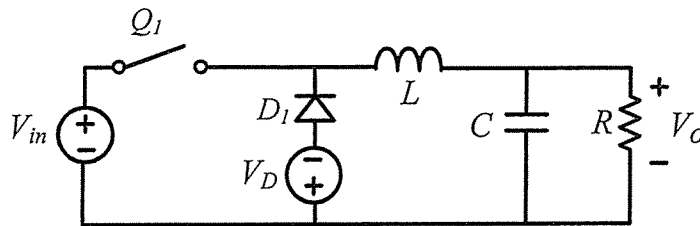


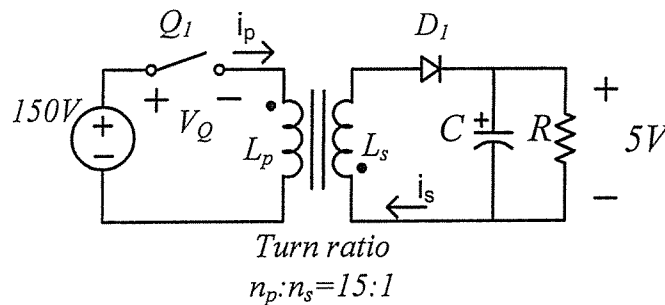1. A DC-DC Buck converter is operating in steady-state. Assuming Q_1 and D_1 are ideal switches. V_D represents diode forward voltage. Output capacitance is very large. Switching frequency is f_s .




- (a) Please derive duty cycle value D of Q_1 as a function of V_{in} , V_D , V_o , and L . Assuming converter operates at continuous conduction mode (CCM). (8%)
- (b) What is the range of R for the converter to operate at CCM? (8%)
2. Given $L_p=100 \mu H$, switching frequency $f_s=200kHz$, $C=500 \mu F$, Output power=25W. Assuming ideal switches.



- (a) Derive duty cycle value D of Q_1 . (6%)
- (b) Sketch the waveforms of V_Q , i_p , and i_s . Indicate important values such as peak and valley values and time values. (12%)
3. 100 KVA, 1200/120 伏特, 60 赫之單相變壓器, 由低壓側激磁而高壓側開路。
 若電源為 120 伏特, 低壓側量得 16 安培電流與 960 瓦特功率。試求
- (a) 功因角。(10%)
- (b) 磁化電流。(7%)
- (c) 鐵心損失分量電流。(6%)

4. 10 馬力，230 伏特，3 相，60 赫之感應電動機，在額定電壓及頻率下，它的滿載轉差率為 4%，試求
- (a) 同步轉速 (以 rpm 表示)。(5%)
 - (b) 滿載轉速 (以 rpm 表示)。(5%)
5. 正弦穩態之平衡三相電力系統，其三相電源電壓，三相輸電線阻抗及三相負載阻抗必須滿足那些條件？(10%)
6. 有一具有兩部發電機之電力系統，其輸電損失可忽略不計，總負載量為 1000MW。假設兩部發電機之發電量分別為 P_1 及 P_2 ，燃料成本分別為 F_1 及 F_2 ，且
- $$F_1 = 460 + 8.28P_1 + 0.00053P_1^2$$
- $$F_2 = 480 + 8.65P_2 + 0.00056P_2^2$$
- 試求 P_1 及 P_2 以使總燃料成本 $F_1 + F_2$ 為最低。(10%)
7. 下圖所示為一平衡三相電力系統之單線圖。假設 $|V_1| = 1.05$ ， $|V_2| = 0.95$ ，輸電線之串聯阻抗 $Z = 0.5 \angle 85^\circ$ ，其並聯電容可忽略不計，令 $\theta_{12} \triangleq \theta_1 - \theta_2$ 。當 $\theta_{12} = 10^\circ$ 時，試求 COMPLEX POWER S_{12} 。(13%)

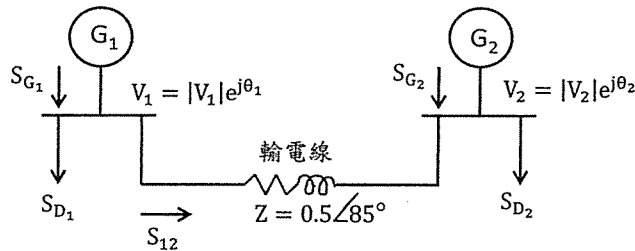

試題隨卷繳回