

1. The LRC network shown in Fig. 1 has $R = 15 \text{ k}\Omega$, $C = 0.4 \text{ }\mu\text{F}$, $L = 1 \text{ mH}$. The current source, I , is a sinusoidal function with fixed amplitude of 2 mA and adjustable frequency. Answer the following questions.

- Determine the resonant frequency of the LRC network in radian frequency. [5]
- What is the quality factor of the LRC network? [5]
- Write down the time domain equation for the inductor current, $i_L(t)$, when the network is operated at resonant frequency. [10]

2. An audio amplifier shown in Fig. 2 is designed to produce $v_{out} = 2K v_{in}$, where K is a constant gain.

- Derive the expression of v_1 and v_2 in terms of K , R , R_a , and v_{in} . [10]
- Derive the expression of R_a in terms of R and K to meet the required output function. [10]

3. The circuit shown in Fig. 3 has DC input voltage $v_s(t) = 10 \text{ V}$, when $t < 0$, and AC input voltage $v_s(t) = \sin t \text{ V}$ when $t > 0$.

- Determine the capacitor voltage $V_c(s)$ in s -domain. [10]
- Determine the capacitor voltage, $v_c(0^+)$, at $t = 0^+$, and the derivative of the capacitor voltage, $v_c'(0^+)$, at $t = 0^+$. [10]

4. Answer the following questions:

- In Fig. 4, find the Norton's equivalent circuit with respect to the terminal a, b. [10]
- What is the maximum power that can be delivered to the load at terminal a, b? [10]

5. A motor is connected to a 240 V , 60 Hz source by a transmission line with resistance $R_{line} = 1 \text{ }\Omega$. The motor would draw 4.8 kW and has power factor $\text{pf} = 0.5$ lagging when operated at 240 V . By adding a parallel-connected capacitor to the motor, the line loss can be reduced.

- Find the equivalent impedance of the motor. [5]
- Determine the capacitance of the parallel-connected capacitor to minimize the line loss. [5]
- Calculate the power supplied by the source before and after the parallel-connected capacitor is installed. [10]

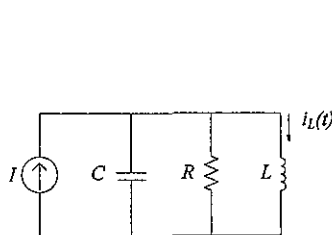


Fig. 1

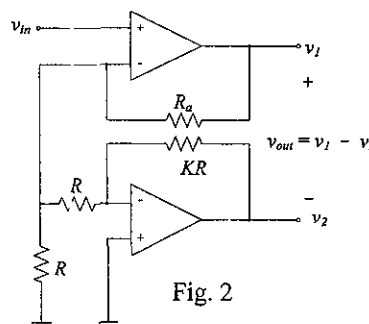


Fig. 2

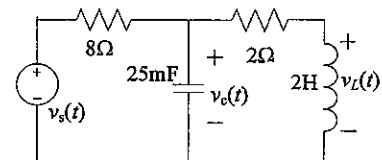


Fig. 3

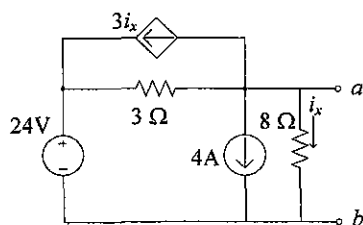


Fig. 4

試題隨卷繳回