

1. (10%) Convert the number  $(54.63)_7$  to binary.
  
2. (15%)
  - (a) (5%) What does the Consensus Theorem in Boolean algebra say? Prove the validity of the theorem.
  - (b) (10%) Use the Consensus Theorem and other Boolean algebra properties to minimize the following sum-of-products Boolean expression  $f$ , and show your minimization steps.


$$f = ADE' + AD' + A'CE' + A'C'E' + BE + B'C'E + CF + EF'$$

3. (15%) Consider the Boolean function  $f(x_1, x_2, x_3, x_4, x_5, x_6)$  over variables  $x_1, x_2, x_3, x_4, x_5, x_6$  with the following (incomplete) function map. Suppose  $f$  can be expressed as a conjunction of two functions  $g(x_1, x_2, x_3)$  and  $h(x_4, x_5, x_6)$ , i.e.,  $f = g \cdot h$ .
  - (a) (5%) How many solutions are there to function  $f$ ?
  - (b) (5%) How many solutions are there to the function pair  $(g, h)$ ?
  - (c) (5%) Show one solution to  $(g, h)$  by expressing  $g$  and  $h$  with their minterm expansions.

		$x_1x_2x_3$							
		000	001	010	011	100	101	110	111
$x_4x_5x_6$	000			0					
	001		1						
	010							1	
	011				1				
	100								0
	101						0		
	110	1							
	111					1			

見背面

 
4. (15%) For the circuit given below, assume all the gates have propagation delay 1 ns.



- (a) (5%) Show the truth table of function  $Z$  in terms of input variables  $A$ ,  $B$ , and  $C$ .
- (b) (5%) Can a static 1-hazard happen in  $Z$ ? If yes, under what condition (that is, fixing  $A$ ,  $B$ ,  $C$  to certain values for enough time and then switching one of the inputs to its opposite value) can it happen?
- (c) (5%) Assume the inputs  $A$ ,  $B$ ,  $C$  and output  $Z$  of the circuit are to be connected to D Flip-Flops, which have setup time 1 ns and propagation delay 0 ns. What is the minimal clock cycle under which the circuit can operate correctly?
5. (20%)
- (a) (10%) Show an FSM example where row matching cannot reduce the number of states to its minimum. (*Row matching* iteratively merges two equivalent states which have the same next state and output for every input.)
- (b) (10%) Prove or disprove that row matching is exact for the state reduction of FSMs corresponding to sequence detectors that reset after every  $k$  inputs for some constant  $k \geq 1$ .
6. (25%) Consider the following block diagram (consisting of a combinational circuit, a control circuit, shift registers, and D Flip-Flops), where “ $Sr$ ” is the start signal of the controller input, “ $Load$ ” the load signal of the controller output, “ $Sh$ ” the shift signal of the controller output, “ $Done$ ” the finish signal of the controller output, “ $SI$ ” the serial data input of shift-registers, “ $Clr$ ” asynchronous clear of the Flip-Flops, “ $CE$ ” the clock enable signal of Flip-Flops. Assume all clock pins are driven by the same clock signal and the two shift-registers have the parallel input loading capability. The circuit compares two 4-bit integers  $A = (a_0, a_1, a_2, a_3)$  and  $B = (b_0, b_1, b_2, b_3)$  in 2’s complement, and sorts them by

placing the larger number in the upper shift-register and placing the smaller one in the lower shift-register. (Assume  $a_3$  and  $b_3$  are the most significant bits of  $A$  and  $B$ , respectively.)

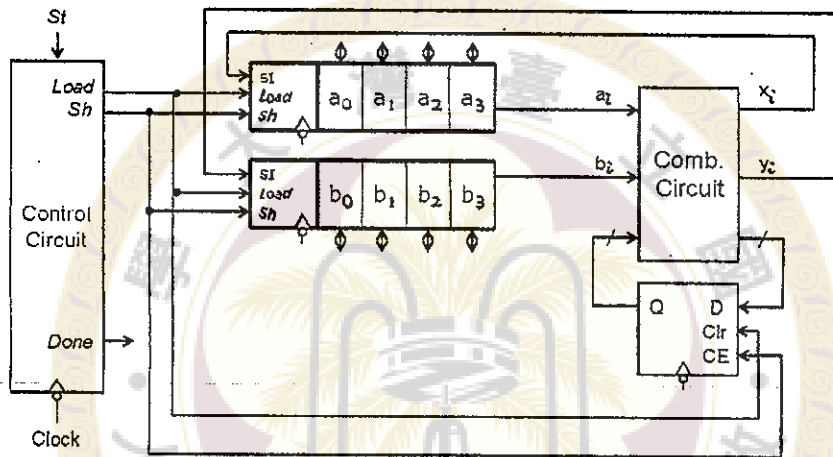- (a) (15 %) Show the state table of the combinational circuit by denoting the states as  $S_0, S_1$ , etc.
- (b) (10 %) Draw the state transition graph of the control circuit. (Assume that the start signal  $S_t$  automatically returns to 0 after one clock cycle.)



試題隨卷繳回