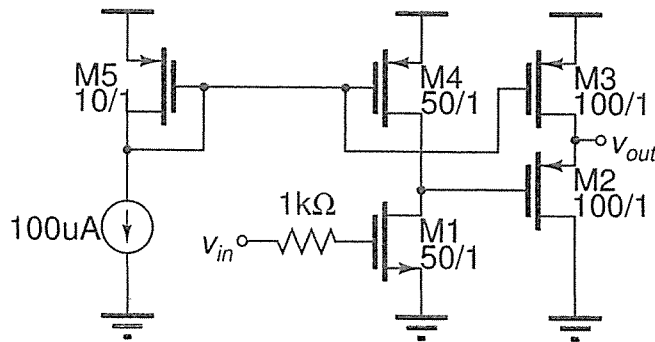


Please show your work leading to your answers. Please also make proper assumptions for your work.

1. (40%) Please find
 - (a) (10%) the DC voltage of V_{in} (neglect channel length modulation effect for DC)
 - (b) (10%) the small-signal voltage gain of the following circuit (v_{out}/v_{in})
 - (c) (10%) the output resistance
 - (d) (10%) the minimum supply voltage required for the following circuit such that all transistors operate in the saturation region.
 $[\mu_n C_{ox}=120\mu A/V^2, \mu_p C_{ox}=50\mu A/V^2, V_{tn}=-V_{tp}=0.7V, \text{ and } \lambda_n=\lambda_p=0.05V^{-1}]$



2. (10%) Please find the resistivity of intrinsic germanium given that $n_i=2.4 \times 10^{13} \text{ cm}^{-3}$, $\mu_n = 3900 \text{ cm}^2/V \cdot s$, and $\mu_p = 1900 \text{ cm}^2/V \cdot s$.
3. (10%) Please draw a CMOS logic implementation of $Y=AB+CD$.
4. (40%) For the following trans-resistance amplifier circuit, Please find
 - (a) (10%) the DC operating point of the transistor (I_{DS} & V_{GS} , neglect λ for DC),
 - (b) (10%) the small-signal gain (v_{OUT}/i_{IN}),
 - (c) (10%) the input resistance R_{IN} ,
 - (d) (10%) the output resistance R_{OUT} .

[note: i_{IN} is a small-signal current source, $\mu_n C_{ox}=120\mu A/V^2$, $V_{tn}=0.5V$, and $\lambda_n = 0.02V^{-1}$]

