


1. Please answer the following questions related to Impedance matching for amplification.

(1) Fill in the following table ( (a) to (h) ) for ideal amplifiers (8%)

Amplifier type	Input impedance	Output impedance	Gain parameters
Voltage	(a)	(e)	$A_{voc}$
Current	(b)	(f)	$A_{isc}$
Transconductance	(c)	(g)	$G_{msc}$
Transresistance	(d)	(h)	$R_{moc}$

- (2) Draw a circuit of a voltage follower using an OP. Using one of the four amplifiers in (1), describe how the voltage follower works (8%)
- (3) Draw a circuit of a current follower using a BJT. Using one of the four amplifiers in (1), describe how the current follower works (8%)
- (4) An amplifier has an output impedance of  $1k\Omega$  and is used to drive an  $8\Omega$  load. We want to use a transformer to allow 50% output power on the load. What is the ratio of turns of the transformer,  $(N_i/N_o)$ ? (4%)

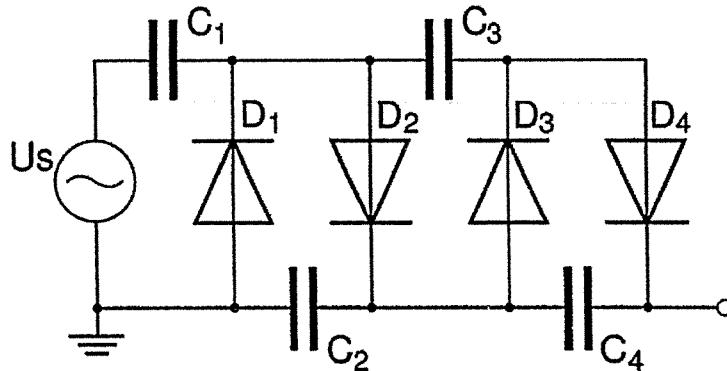2. Please analysis the following circuit.




Initially, all capacitors are all fully discharged. All diodes and capacitors are ideal. The AC source,  $U_s$ , is  $V\sin(\omega t)$ . Please answer the following questions

- (1) When  $t = \pi/2\omega$ , calculate the voltages of the left side and right side for  $C_1$  to  $C_4$ . (8%)
- (2) When  $t = 2\pi/\omega$ , calculate the voltages of the left side and right side for  $C_1$  to  $C_4$ . (8%)
- (3) Electrolyte capacitors are used for  $C_1$  and  $C_4$ . Assign polarity and voltage rating all of them. (12%)

見背面

3.

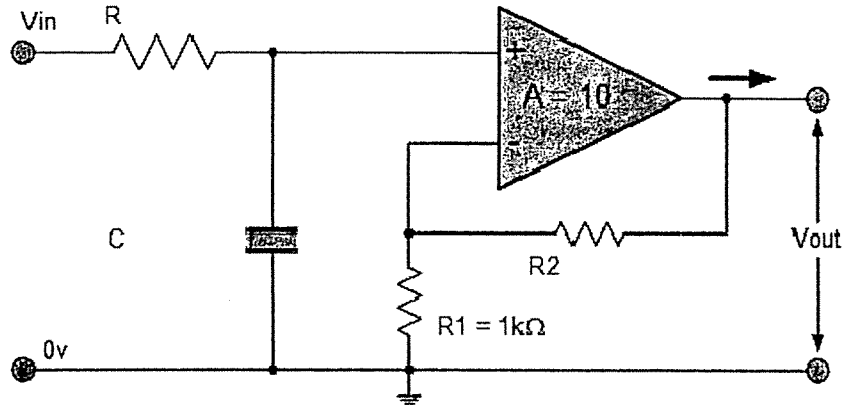(1) Design a non-inverting active low pass filter circuit that has a gain of ten at low frequencies, a high frequency cut-off or corner frequency of 159Hz and an input impedance of 10KΩ. Please assign the values of R2 and C. (5%)



(2) Design a simplified non-inverting amplifier filter circuit with a C location different from (1). Draw the circuit with component values assigned. (6%)

(3) Design an equivalent inverting amplifier filter circuit. Draw the circuit with component values assigned. (6%)

(4) Following (3), what does the circuit become if the feedback resistance is removed? (2%)

4. Consider the circuit shown below:

(a) Derive an expression for the transfer function  $H(f) = V_{out} / V_{in}$ . (5%)

(b) Derive an expression for the resonant frequency of this circuit. (5%)

(c) What type of the filter the transfer function  $H(f)$  is? (5%)

(d) Draw the Bode plot for the magnitude of the transfer function  $H(f)$  when  $R = 10 \Omega$ ,  $L = 10 \text{ mH}$ , and  $C = 0.02 \mu\text{F}$ . (5%)

(e) Draw the plot for the impedance magnitude the source voltage  $V_{in}$  sees. (5%)

