

※ 共二部份，第一部份為填充題，請將答案填於答案卷上；第二部份為計算問答題，請寫出算式，並請依序作答。

第一部份：填充題 (15 pt)

1. Memory (row-address decoder): (6 pt)

(a) (4 pt)

Assume there are 5 bits in the row addresses, there are (A) word lines. By using NOR gate array with Boolean operation such as $W_i = \overline{A_0 + \dots + A_j}$ (Fig. 1(a)), you will need (B) NMOS transistors to implement this decoder. Note: the figure shows the 3-bit NOR decoder structure. Make the analogy for 5-bit case.

(b) (2 pt)

If now you'd like to reduce the transistor counts, you can use a tree structure (Fig. 1(b)) to cut down the number to (C).

 


Fig. 1 (a)

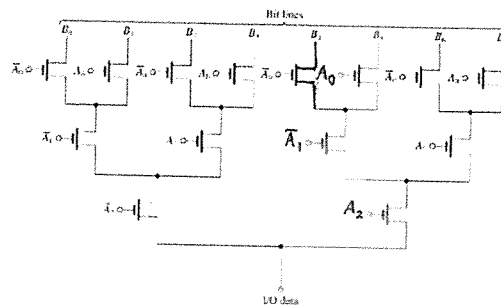


Fig. 1 (b)

2. BJT Basics: (6 pt)

(a) (2 pt)

There are two bias conditions: forward and reverse biases. For a BJT (n-p-n) device to be an amplifier (operated in the active region), you need a (D) biased base/emitter junction and a (E) biased base/collector junction.

(b) (2 pt)

There are two type of carriers: electrons and holes. The carriers representing output signals (collector current, I_C) in an n-p-n BJT are (F). The carriers representing input signals (base current I_B) in an n-p-n BJT are (G).

(c) (2 pt)

There are two mechanisms for carrier transport: drift and diffusion. The current in a BJT is dominated by (H). The current in a MOSFET is dominated by (I).

3. OP AMP: (3 pt)

(a) (1 pt)

For an open-loop OP AMP circuit, when you have an input voltage difference ($V_{in} = V_+ - V_-$) with a gain A of OP AMP, you will get output $V_{out} =$ _____.

(b) (2 pt)


For a closed-loop OP AMP circuit, you usually assume the voltages at negative and positive terminals of OP AMP are the same. If so, $V_{in} = V_+ - V_- \sim 0$ and $V_{out} = A(V_+ - V_-)$ will be 0, too. Right or wrong? (No need to explain).

第二部份：計算問答題 (85 pt)

4. Oscillator/Filter: (16 pt)

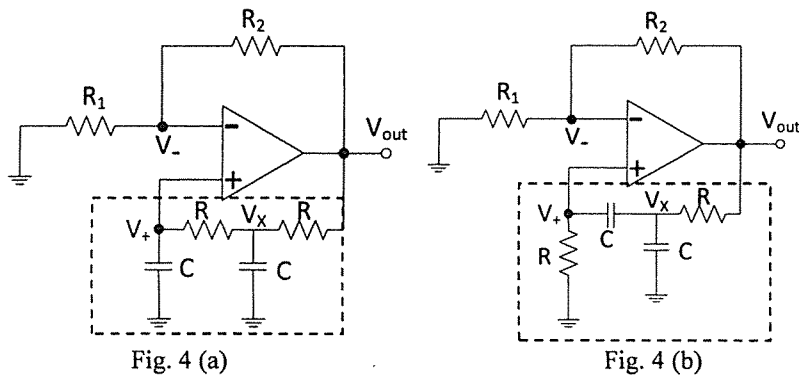(a) (12 pt)

Please derive the feedback network gain $\beta \equiv \frac{V_+}{V_{out}}$ (which is enclosed in the dash rectangles) for the circuits in Fig. 4 (a) and (b)



(b) (4 pt)

Which circuit will oscillate and what is the oscillation frequency ω ?

5. MOSFETs (40 pt)

A common source amplifier is plotted in Fig. 5-1 (a) with its VTC shown in Fig. 5-1 (b). The DC bias parameters: $V_{DD} = 1.8$ V, $R_D = 17.5$ k Ω , $V_{th} = 0.4$ V, $k_n = 4$ mA/V², and ignore the channel length modulation effect.

 


Fig. 5-1

(a) (8 pt)

Determine the values of V_{GS} and V_{DS} at point A and B in Fig. 5-1 (b). Hint: for point A, NMOS is just turned on ($V_{GS} = V_{TH}$). For point B, the NMOS is operated at the boundary of the saturation and triode modes.

- (b) (12 pt)
 What are current values (I_D) at point A and B? What are g_m values at point A and B? What are voltage gain A_v ($\equiv \frac{V_{DS}}{V_{GS}}$) at point A and B?
- (c) (4 pt)
 What are noise margins for low (NM_L) and high inputs (NM_H)? (Hint: you don't need to calculate the exact values of V_{IL} and V_{IH} at slope = -1, but approximately use $V_{OL} \sim 0$, $V_{IL} = V_{th}$ and $V_{IH} = V_{GS}$ at point B in Fig. 5-1(b)).
- (d) (16 pt)
 At which input state (ON or OFF), static power is consumed (i.e. current flows)? ON state: $V_{GS} = V_{DD}$; OFF state: $V_{GS} = 0$. What is the output voltage (V_{DS})? How much is the current? What is the average static power? (Hint: assume half of the period is operated at both ON and OFF states exactly).

6. Active filter: (29 pt)

For a feedback loop system shown in Fig. 6-1(a), the loop gain is $L(s) = At(s)$ and the characteristic equation is $1 + L(s) = 0$. RC network $t(s)$ is defined in Fig. 6-1 (b).

 


Fig. 6-1

- (a) (3 pt)
 To get poles of the entire system with a characteristic equation above, you can actually calculate the zeros of the RC network. Please explain mathematically.
- (b) (8 pt)
 Please derive $t(s) (\equiv \frac{V_a}{V_b})$ in terms of s for the circuit in Fig. 6-2.

 


Fig. 6-2

 


Fig. 6-3

見背面

(c) (6 pt)

You can translate the original feedback loop in Fig. 6-1 (a) to that in Fig. 6-3. Please show that these two loops are equivalent.

(d) (6 pt)

Based on the concept in (c), we can transform the circuit in Fig. 6-4 (a) to that in Fig. 6-4 (b). Please place the 4 components (R_1 , R_2 , C_3 , and C_4) in the right position on Fig. 6-4 (b). Please place the negative and positive input symbols into the two input terminals of the OP AMP.

 


Fig. 6-4

(e) (6 pt)

Based on (d), by injecting an input signal from one of the ground terminal in Fig. 6-5, what type of the filter do you have? Low-pass or high-pass? Please explain.

 


Fig. 6-5

試題隨卷繳回