
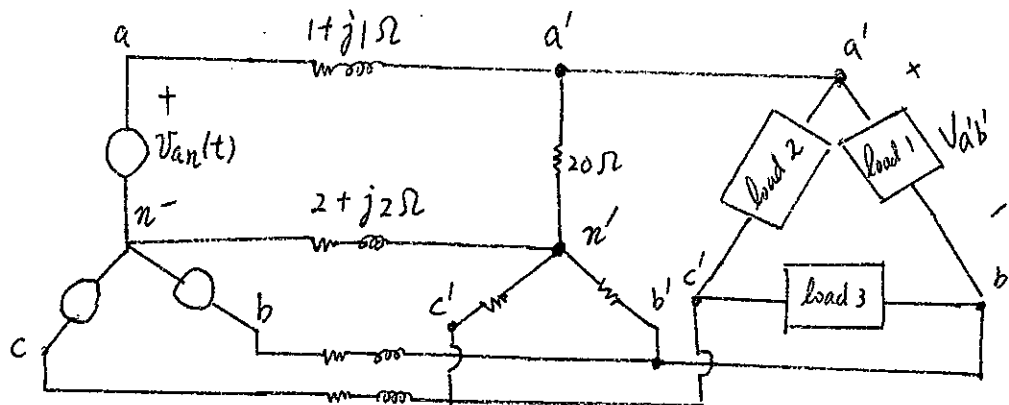


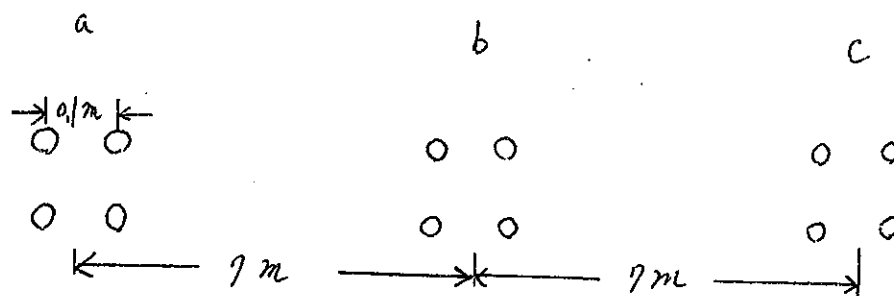
1. Given the 60 Hz, balanced three-phase system shown below, find $V_{an}(t)$ when each of the three loads (load1, load2, load3) consumes $P = 500$ W at a power factor of 0.85 lagging and $V_{a'b'} = 100\sqrt{3} \angle 30^\circ$ V. (12%)



2. Find the per phase inductance in H/m and per phase capacitance to neutral in F/m for the following 345 KV, 60 Hz, completely transposed, balanced three phase line. Assume that the radius of each sub-conductor is 1 cm. (10%)



3. For the system shown below, all quantities are per phase values. Assume that $-90^\circ \leq \angle V_2 \leq 90^\circ$. Pick Q_{G2} so that $|V_2| = 1.03$. (11%)

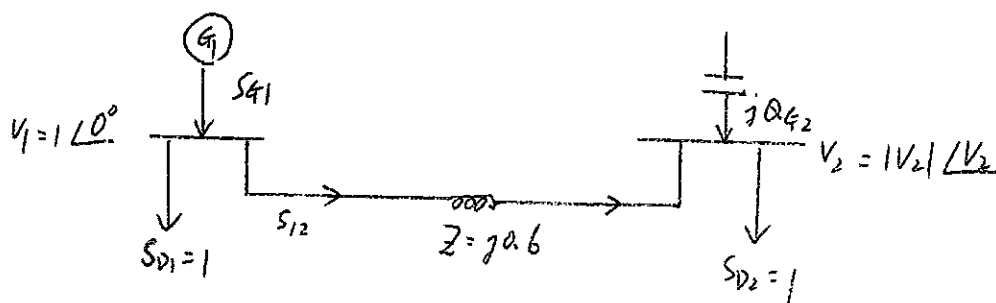

見背面

4. A magnetic circuit with a single air gap is shown in Fig.1. The core dimensions are:

$$A_c = 1.8 \times 10^{-3} \text{ m}^2, l_c = 0.6 \text{ m}, g = 2.3 \text{ mm}, N = 83 \text{ turns}$$

Assume that the core is of infinite permeability ($\mu \rightarrow \infty$) and neglect the effects of fringing fields at the air gap and leakage flux.

- (8%) Calculate the reluctance of the core R_c and that of the gap R_g .
- (8%) For a current of $i = 1.5 \text{ A}$. calculate the total flux ϕ , the flux linkages λ of the coil, and the coil inductance L .


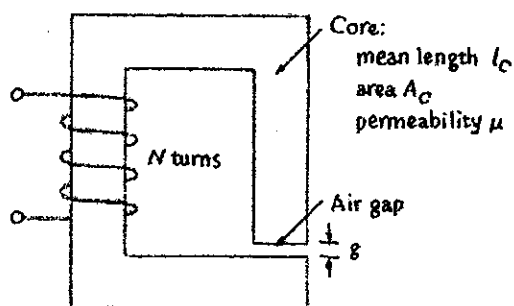


Fig. 1


- (8%) For a 24 poles AC rotating machine, if the magnetic field speed is 300rpm (rotation per minute), what is the frequency of stator current?
- (9%) If a three-phase induction motor operated by 3ϕ , 110V, 60Hz AC source has a slip rate $s = 1\%$, then find the frequency of rotor winding voltage.

接次頁

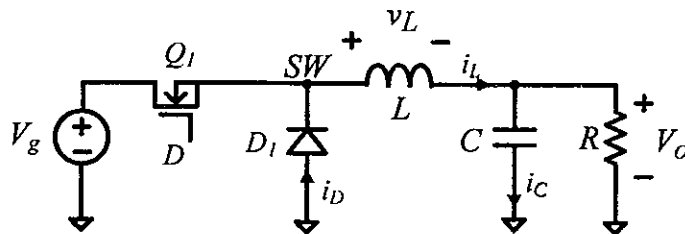7. A buck converter below operates at steady-state. Assume the converter is ideal except diode D_1 has a 1V forward voltage drop. $V_g = 10V$, $V_o = 5V$, $L = 100\mu H$, C is very large, Switching frequency $f_s = 100kHz$, Output Resistance $R = 0.5 \text{ ohm}$.



- Derive the input to output dc gain (V_g/V_o) as a function of duty cycle D . (5%)
 - Sketch the time waveforms of D , SW voltage, i_L , i_D . Mark peak and valley values (8%)
 - Derive the root-mean-square (rms) value of i_L . (3%)
 - Determine the inductance of L if the converter is operating at the boundary conduction mode when $R = 5 \text{ ohm}$. (4%)
8. Answer below questions. Explanation or mathematic derivations are required.
- What is the value of integration of inductor voltage across a switching period at steady-state? (3%)
 - Draw the two equivalent circuits during active switch turn-on and turn-off, respectively, of the Flyback converter below. (Hint: use ideal transformer model; consider the magnetizing inductance of a real transformer; use short circuit and open circuit to express a switch in on and off state, respectively.) (4%)

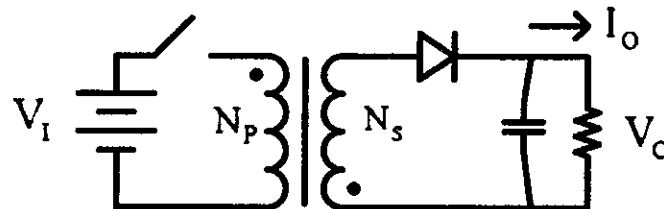

- Name one property difference of the real transformer in problem (b) compared with an ideal transformer model. (3%)
- Draw the Bode plot (gain and phase plots) of the transfer function $T = \frac{10(s-10)}{s+1000}$ (4%)

試題隨卷繳回