
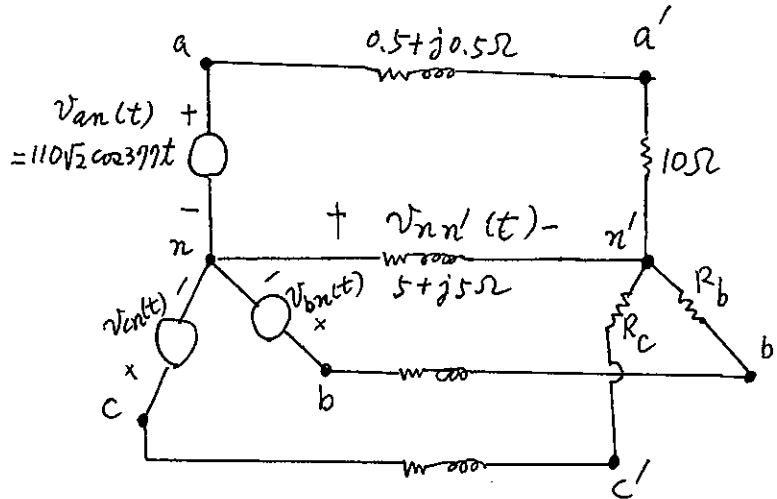


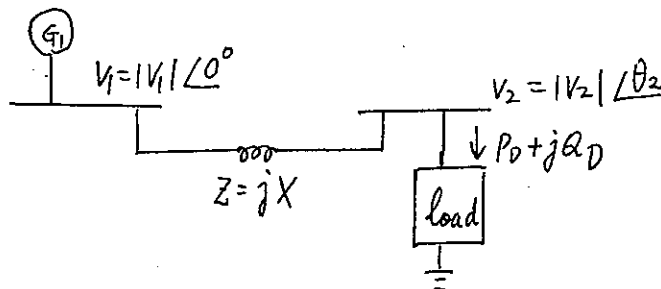
1. Find  $R_b$ ,  $v_{bn}(t)$ , and  $v_{n'n}(t)$  for the balanced negative-sequence three phase system shown below. (9%)



2. Let  $|V_1| = 1.03$ ,  $X = 0.3$ ,  $P_D = 0.3$ . Find  $|V_2|$  when load power factor is 0.97 lagging. (12%)




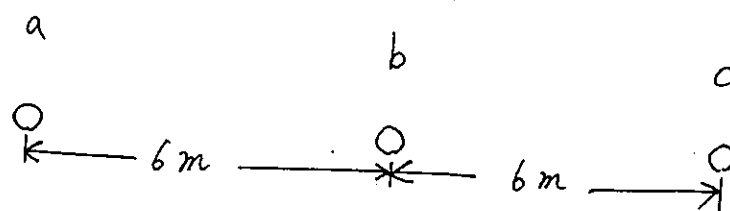3. Consider the 60 Hz, 345 KV, completely transposed, balanced three phase lines as shown below. The radius of each conductor is 1.1 cm. Find the per phase inductance in H/m and per phase capacitance to neutral in F/m. (12%)



見背面

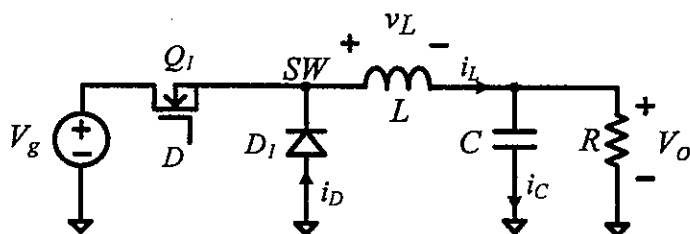4. A buck converter below operates at a steady state. Assume the converter is ideal except switch  $Q_1$  has a 1V forward voltage drop during turn-on.  $V_g = 10V$ ,  $V_o = 1V$ ,  $L = 100\mu H$ ,  $C$  is very large, Switching frequency  $f_s = 100kHz$ , Output Resistance  $R = 0.1\text{ ohm}$ .




- Please define the "steady state" of a converter. (3%)
  - Derive the input to output dc gain ( $V_g/V_o$ ) as a function of duty cycle  $D$ . (5%)
  - Sketch the time waveforms of  $D$ ,  $SW$  voltage,  $i_L$ ,  $i_C$ . Mark peak and valley values (9%)
  - At what value of  $R$  will the converter operate at the boundary conduction mode? (4%)
  - Assume the switching network ( $Q_1$  and  $D_1$ ) of the buck converter is modified and  $SW$  voltage is connected to  $2V_g$  during on-time and  $V_g$  during off-time. Please derive the input to output dc gain ( $V_g/V_o$ ) as a function of duty cycle  $D$ . (6%)
5. Answer the below questions. Explanation or mathematic derivations are required.
- Why the integration of the capacitor current over a switching period at steady-state is zero? (3%)
  - Draw the Bode plot (gain and phase plots) of the transfer function  $T = \frac{1}{s+1000}$  (4%)

接次頁

6. 一交流旋轉電機共有極數 24 極，若轉子轉速為 300rpm(rotation per minute)，則定子電流頻率為幾 Hz?(20%)

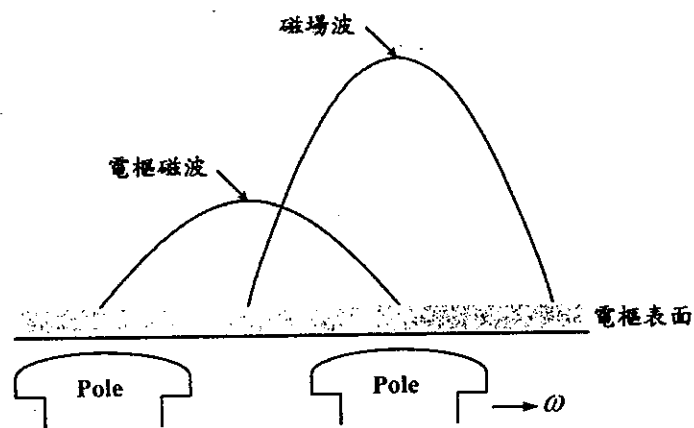7. 請畫出以下圖同步機之  $E_{af}$ 、 $I_a$ 、 $\Phi_f$  相量圖(Phasor diagram)，並解釋之。(13%)



試題隨卷繳回