

- (16%) In Fig. 1, please calculate the value of  $R_{out}$  for maximum power, and determine the maximum power absorbed by  $R_{out}$ .
- (14%) In Fig. 2, please find  $v_{out}$  if  $v_1$  equals  $-5$  V.

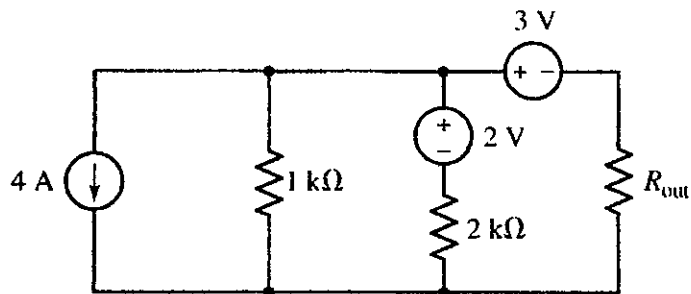


Fig. 1.

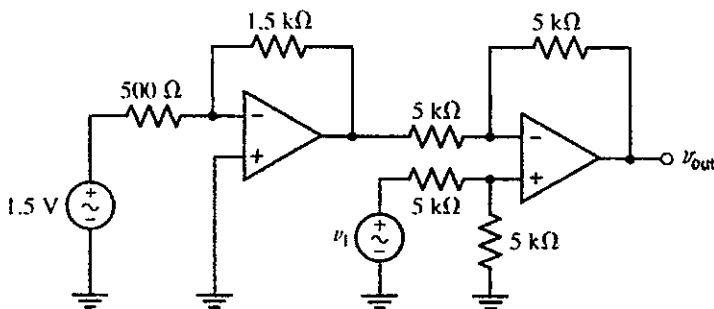


Fig. 2.

- (24%) In Fig. 3, let  $i_s = 60e^{-200t}$  mA with  $i_1(0) = 20$  mA. (a) Find  $v(t)$  for all  $t$ . (b) Find  $i_1(t)$  for  $t \geq 0$ . (c) Find  $i_2(t)$  for  $t \geq 0$ .
- (12%) Please plot the input/output characteristics of the circuits depicted in Figs. 4(a) and 4(b) using an ideal model for the diodes. Assume  $V_B = 2$  V.

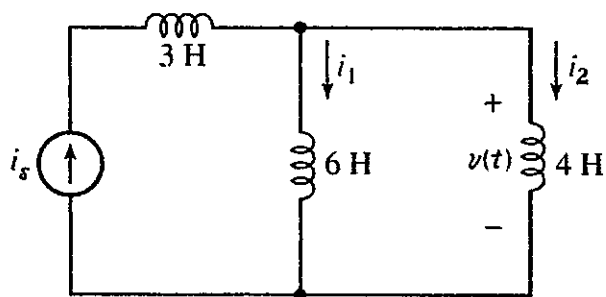


Fig. 3.

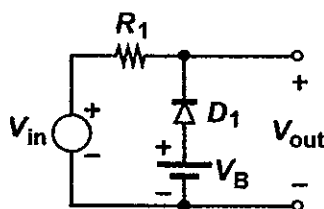


Fig. 4(a).

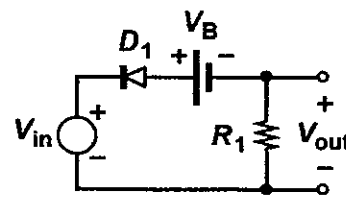


Fig. 4(b).

- (16%) The transistor in Fig. 5 is biased with a constant current source  $I = 1$  mA and has  $\beta = 100$  and  $V_A = 100$  V. Please calculate the overall voltage gain  $v_y/v_{sig}$ .
- (18%) The NMOS and PMOS transistors in the circuit of Fig. 6 are matched with  $k'_n(W_n/L_n) = k'_p(W_p/L_p) = 1$  mA/V<sup>2</sup> and  $V_{tn} = -V_{tp} = 1$  V. Assuming  $\lambda = 0$  for both devices, find the drain currents  $i_{DN}$  and  $i_{DP}$  and the voltage  $v_O$  for  $v_1 = 0$  V,  $+2.5$  V, and  $-2.5$  V.

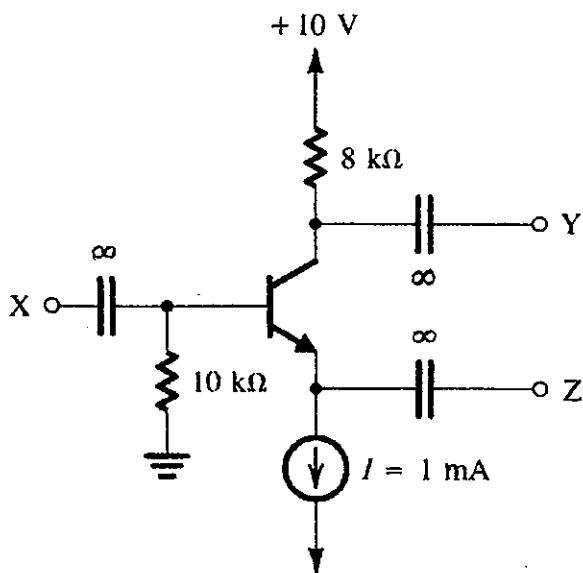


Fig. 5.

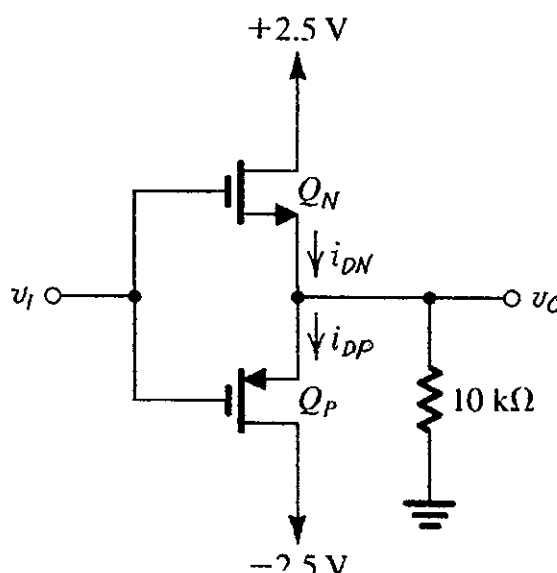


Fig. 6.