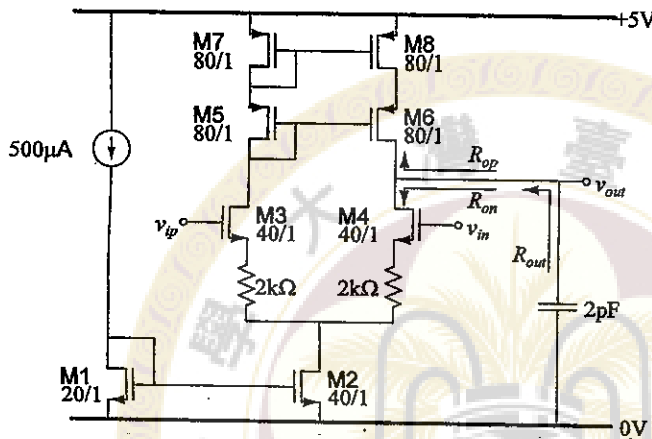



1. (50 分) For the following amplifier:

- (a) Find the slew rate of the amplifier. (10 分)
- (b) Find the output resistances  $R_{op}$ ,  $R_{on}$ , and  $R_{out}$ . (30 分)
- (c) Find the small-signal voltage gain  $(v_{out}/(v_{ip}-v_{in}))$  (10 分)

[Please ignore channel length modulation effect when calculating bias currents, assume all transistors are biased correctly in the saturation region, and assume  $\mu_n C_{ox}=100\mu A/V^2$ ,  $\mu_p C_{ox}=50\mu A/V^2$ ,  $V_m = -V_{tp} = 0.5V$ , and  $\lambda=0.05V^{-1}$ ]



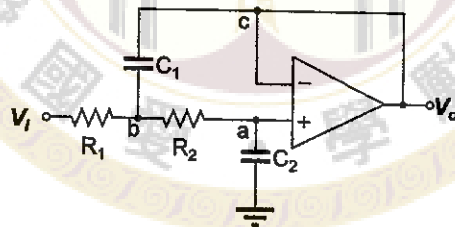2. (30 分) The following circuit is a second-order low-pass filter. (a) Please find the transfer function  $[V_o(s)/V_i(s)]$  in terms of  $R_1$ ,  $R_2$ ,  $C_1$ ,  $C_2$ , and  $s$ . (b) Assume  $R_1=R_2=10k\Omega$ , please find  $C_1$  and  $C_2$  such that the filter is a second-order butterworth low-pass filter with a 3-dB cutoff frequency of 2MHz.



3. (20 分) Please find the small-signal voltage gain  $(v_{out}/v_{in})$  and output resistance ( $R_{out}$ ) for the following circuit. [assume  $W/L=15$ ,  $\mu_p C_{ox}=50\mu A/V^2$ ,  $V_{tp} = -0.5V$ ,  $\lambda=0.05V^{-1}$  for the PMOS transistor and  $|V_A|=50V$ ,  $\beta=200$  for the NPN transistor]

