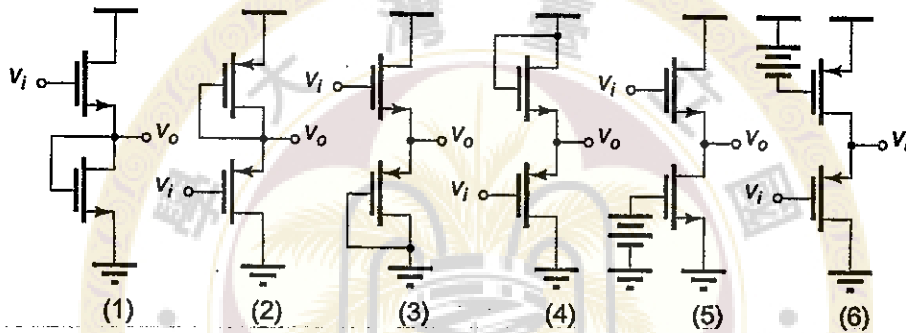


1. (50 分) The following six circuits are variations of the source follower. Assume $\mu_n = 2\mu_p$, $\lambda_p = 2\lambda_n \ll 1$, the W/L ratios and bias currents are the same for all transistors, and the supply voltage (V_{DD}) are the same for all amplifiers. Please find the circuit(s) with the following characteristics:

- (a) Highest small-signal voltage gain (12 分)
- (b) Lowest-small signal voltage gain (12 分)
- (c) Highest output resistance (13 分)
- (d) Lowest output resistance (13 分)

Please neglect bulk effect and assume that no load resistors are connected at the outputs.



2. (50 分) Assume $\mu_n C_{ox} W/L = 1600 \mu A/V^2$, $V_T = 0.5V$, and $\lambda = 0.01$ (neglect λ for (a)~(c)) for all transistors in the following circuit. Please find:

- (a) The value of R such that the output voltage ($v_{o+} - v_{o-}$) has zero DC offset (12 分)
- (b) The input common-mode range (ICMR) (12 分)
- (c) The small-signal differential gain [Hint: find gain of two differential half circuits] (13 分)
- (d) The common-mode rejection ratio (CMRR) (13 分)

