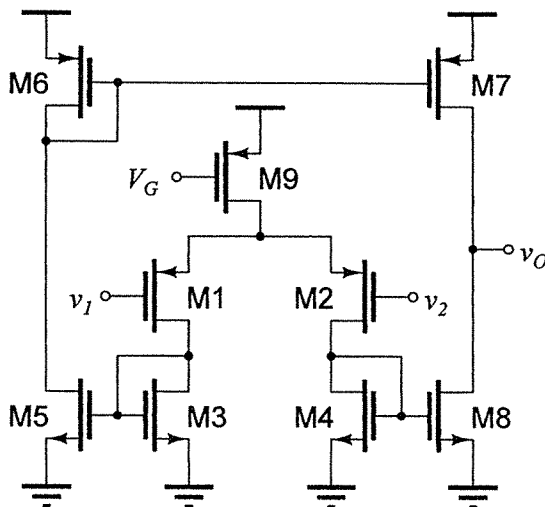


Please show your work leading to your answers. Please also make proper assumptions for your work.

Assume $\mu_n C_{ox} = 120 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 50 \mu\text{A}/\text{V}^2$, $V_{tn} = -V_{tp} = 0.7 \text{ V}$, $\lambda_n = \lambda_p = 0.05 \text{ V}^{-1}$, and a supply voltage of 5 V. The transistor sizes (W/L) are all $10 \mu\text{m}/1 \mu\text{m}$, and the quiescent current is $40 \mu\text{A}$ for the following CMOS operational amplifier (OPA).



- (10%) What is the non-inverting input of the OPA? (v_I or v_2)
- (10%) What is the bias voltage V_G ? (Please neglect channel length modulation effect.)
- (10%) What is the input resistance of the OPA?
- (10%) What is the output resistance of the OPA?
- (10%) What is the small-signal gain of the OPA ($v_O/|v_I - v_2|$)?
- (10%) What is the slew rate if the OPA has a load capacitance of 10 pF at v_O ?
- (10%) What is the maximum input common-mode voltage ($V_{CM\text{max}}$) of the OPA?
- (10%) What is the minimum input common-mode voltage ($V_{CM\text{min}}$) of the OPA?
- (10%) What is the unity gain bandwidth of the OPA if the load capacitance is 10 pF at v_O ?
- (10%) What is the total power dissipation of the OPA when the output voltage (v_O) is 2.5 V and the load is a 10 pF capacitance.

試題隨卷繳回