

- The circuit shown in Figure 1 has two sources, $i(t) = 2\cos(20t+180^\circ)$ A and $v(t) = 80\cos(20t)$ V.
 - Determine the inductor current $i_L(t)$ and the resistor current $i_R(t)$. [20]
 - Draw the phasor diagram of the inductor and resistor currents. [5]

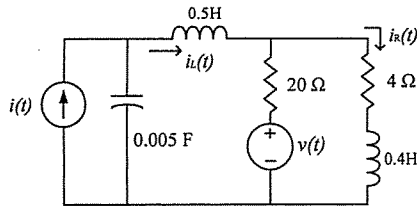


Figure 1

- The circuit shown in Figure 2 has two voltage sources. $v_1(t) = 4u(t)$ V where $u(t)$ is the unit step function ($u(t)=0$ for $t<0$ and $u(t)=1$ for $t\geq 0$). $v_2(t) = 1$ V for $t<0$ and is disconnected (removed) from the circuit at $t = 0$. Please determine the capacitor voltage $v_C(t)$ for $t>0$. [25]

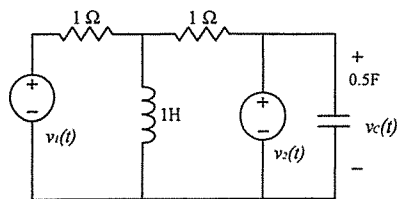


Figure 2

- Construct the asymptotic Bode plot of the **gain** and **phase** for the transfer function :

$$H(s) = \frac{100s \cdot (50 + s)}{(400 + s)(100 + s)^2} \quad (\text{Note: critical points and slopes must be specified}) \quad [25]$$

- A difference amplifier using an ideal operational amplifier powered by ± 12 V is shown in Figure 3. The resistor values ($R_1, R_2, R_3,$ and R_4) and input voltages ($v_1(t)$ and $v_2(t)$) for different operation cases are shown in Table A. Please determine the output voltage $v_o(t)$ for Case 1 and Case 2. [25]

Table A

	R_1 (Ω)	R_2 (Ω)	R_3 (Ω)	R_4 (Ω)	$v_1(t)$ V	$v_2(t)$ V
Case 1	110k	660k	220k	440k	5.2	0.8
Case 2	100k	110k	440k	800k	7.6	0.4

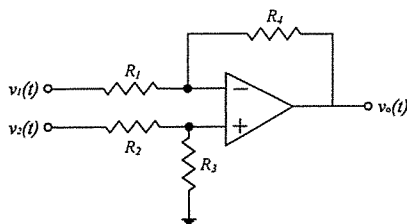


Figure 3

試題隨卷繳回