

*請依題號順序作答

A. (25%) Please answer the following questions in few sentences and/or drawings

1. Please explain the principle of superposition briefly. (5%)
2. Please list 5 physical limitations of operational amplifiers and explain them briefly. (10%)
3. Please list a noise coupling mechanism and explain it briefly. (5%)
4. Please explain the gain-bandwidth product in filter design. (5%)

B. (75%) Calculations

1. Wheatstone bridge circuit shown in Fig. 1 has been applied in many applications. Please find the value of the voltage $V_{ab} = V_a - V_b$. in terms of resistors and V_s . (10%)

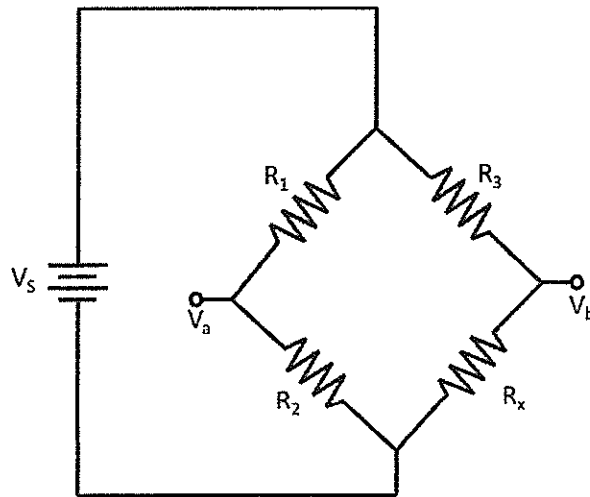


Figure 1.

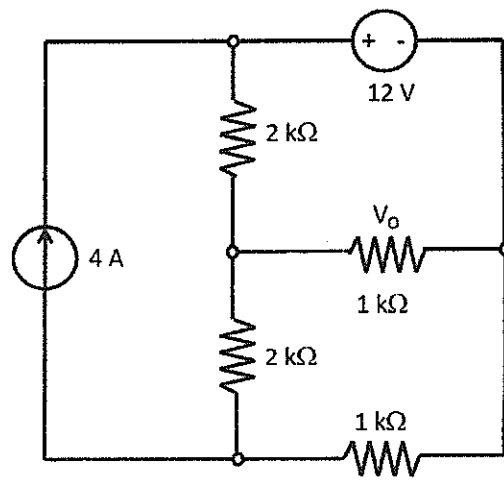


Figure 2.

2. Please find V_o in the circuit shown in Fig. 2 (10%)
3. Assume the op-amp is ideal for this problem. As shown in Fig. 3, determine an expression for, and numerical value of the output voltage. (15%)

$$v_{S1} = 2.9 \times 10^{-3} \cos(\omega t) \text{ V}; v_{S2} = 3.1 \times 10^{-3} \cos(\omega t) \text{ V};$$

$$R_1 = 1\text{k}\Omega; R_2 = 3.3\text{k}\Omega; R_3 = 10\text{k}\Omega; R_4 = 18\text{k}\Omega;$$

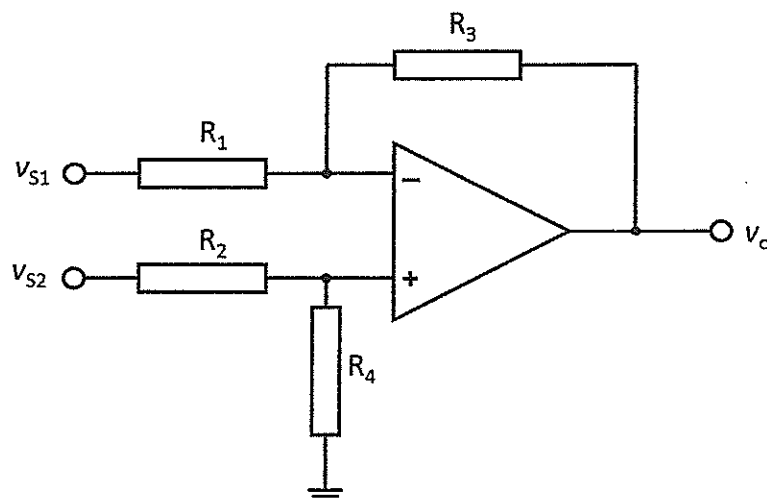


Figure 3

見背面

4. In the circuit shown in Fig. 4, assume that DC steady-state condition exist for $t < 0$. Determine at $t = 0+$, just after the switch is opened, the current through and voltage across the inductor and the capacitor and the current through R_{S2} . (20%)

$V_{S1} = 15\text{ V}; V_{S2} = 9\text{ V}; R_{S1} = 130\Omega; R_{S2} = 290\Omega; R_1 = 1.1\text{ k}\Omega; R_2 = 700\Omega; C = 0.35\mu\text{F}$

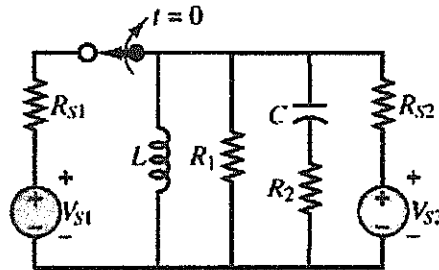


Figure 4.

5. The circuit in Fig. 5 is a common-emitter amplifier, where C_{C1} and C_{C2} are coupling capacitors. (20%)
- (1) For a MOSFET with a threshold voltage of V_t , derive the maximum voltage gain for given V_{DD} and V_{GG} . (6%)
 - (2) Given that $V_{DD} = 5\text{ V}$, $V_{GG} = 2\text{ V}$, $k_n = 2\text{ mA/V}^2$ and $V_t = 1\text{ V}$, find the maximum voltage gain of the amplifier and the value of R_D in this case. (6%)
 - (3) A sinusoidal output with an amplitude of 1 V is needed for the amplifier. Using the same V_{DD} , V_{GG} , k_n and V_t in (2), find the maximum voltage gain and the value of R_D . (8%)

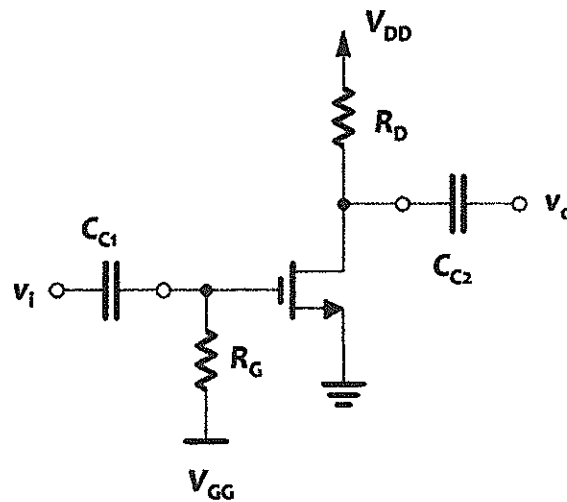


Figure 5.

試題隨卷繳回