

1. Find the Norton equivalent of the network at terminal A-B in Figure 1. [10]
2. A periodic pulsating current source,  $i(t)$ , is applied to a  $12\ \Omega$  resistor as shown in Figure 2. Please determine a) the average current  $I_{avg}$ , b) the rms current  $I_{rms}$ , and c) the power absorbed by the  $12\ \Omega$  resistor. [15]
3. Use **superposition** to find the output voltage  $V_o$  in Figure 3. [25]
4. The ideal switch in Figure 4 is opened at  $t=0$ . Please determine the inductor current  $i_L(t)$  for  $t>0$ . [25]
5. Two motors, M1 and M2, are operated the  $240\text{V}_{rms}$ ,  $60\text{Hz}$  as shown in Figure 5. The M1 consumes  $36\text{ kW}$  with power factor  $0.82$  lagging, and the M2 consumes  $48\text{ kW}$  with power factor  $0.88$  lagging. The transmission line impedance is  $(0.1+j0.3)\ \Omega$ . a) Determine the demanded input voltage source  $V_s$ , b) Find the power factor at the load terminal A-B. c) Determine the capacitance,  $C$ , that can be connected to the load terminal to improve the load terminal power factor to  $0.95$  lagging. [25]

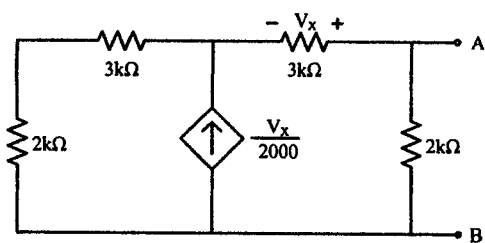


Figure 1

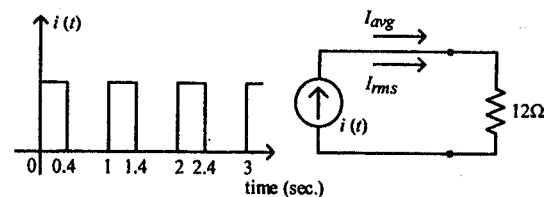


Figure 2

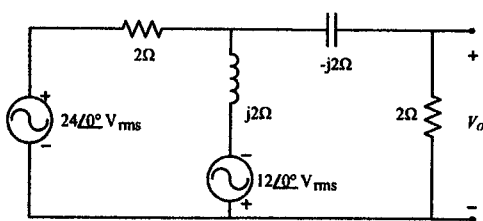


Figure 3

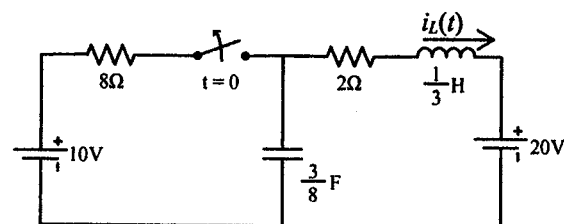


Figure 4

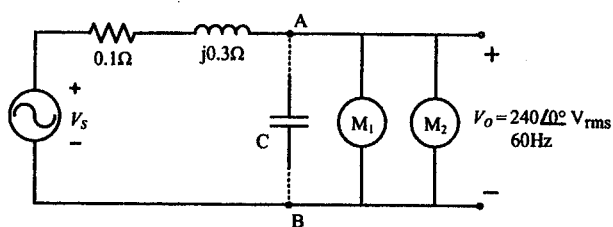


Figure 5

試題隨卷繳回