


題號： 246
 科目： 電子學(A)
 節次： 2

國立臺灣大學 110 學年度碩士班招生考試試題

題號： 246
 共 1 頁之第 1 頁

Assume $\mu_n C_{ox} = 120 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 50 \mu\text{A}/\text{V}^2$, $V_m = -V_{tp} = 0.7 \text{ V}$, $\lambda_n = \lambda_p = 0.02 \text{ V}^{-1}$, and a supply voltage of 5 V for the following CMOS operational amplifier (OPA).

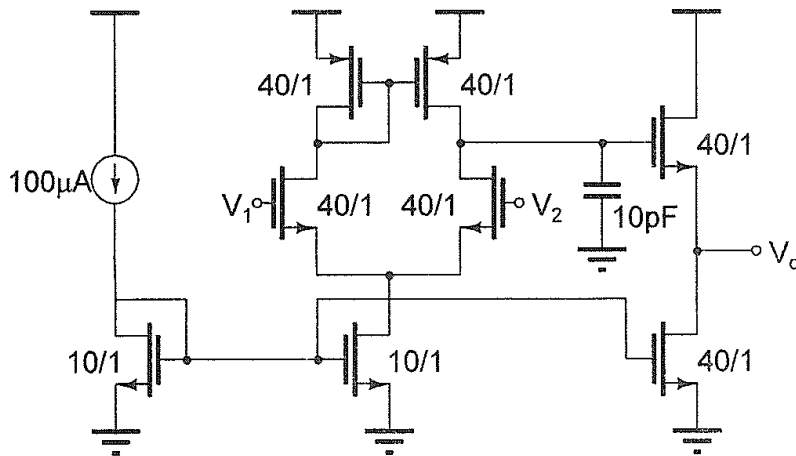1. (20%) Identify the non-inverting input node (V_1 or V_2)
2. (10%) What is the input resistance of the OPA?
3. (10%) What is the output resistance of the OPA?
4. (10%) What is the small-signal voltage gain of the OPA?
5. (10%) What is the maximum input common mode range (ICMR) of the OPA (neglect channel length modulation effect)?
6. (10%) What is the minimum input common mode range (ICMR) of the OPA (neglect channel length modulation effect)?
7. (10%) What is the 3-dB bandwidth of the amplifier?
8. (10%) What is the unity gain bandwidth of the amplifier?
9. (10%) If a load capacitance (C_L) is connected to the node V_o , what capacitance would result in a phase margin of 45 degrees? (neglect internal capacitances of transistors)



試題隨卷繳回