

1. a) Please explain what is the Thevenin's theorem [5] and provide the proof of that. [10]
2. Use superposition to find  $V_1$  in the circuit of Figure 1. [15]
3. For the circuit shown in Figure 2 with input voltage  $V_{in}=3V$ , please determine the output voltage  $V_o$  under the following conditions: a) the op-amp is ideal [5]; b) the op-amp is not ideal and has the following parameters: input resistance  $R_i=500k\Omega$ , output resistance  $R_o=200\Omega$ , and voltage gain  $A_v=2 \times 10^4$ . [15]
4. A  $10V_{rms}$  sinusoidal AC voltage source is supplying the power to a series connected RLC network with  $R=0.2\Omega$ ,  $L=20\mu H$ , and  $C=5\mu F$ . Please determine the expression of energy,  $E_L(t)$ , stored inside the inductor L if the frequency of the voltage source is: a) 60Hz: b) 16kHz. [10]
5. For the circuit shown in Figure 3, a  $1\Omega$  resistor is shorted by closing the switch at  $t=0$ . Please determine the inductor current  $i_L(t)$  for  $t>0$ . [20]
6. The s-domain transfer function of a complex network can be expressed as:  $H(s) = \frac{s+10}{s^2+s}$ . Please draw the bode plots (both magnitude and phase) of  $H(s)$ . Please clearly mark those critical points and the slopes of those curves. [20]

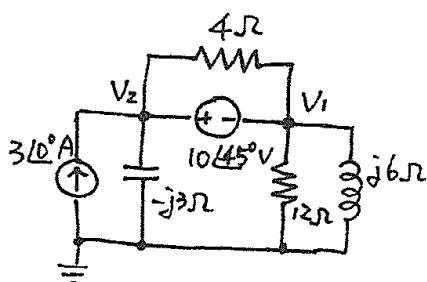


Figure 1

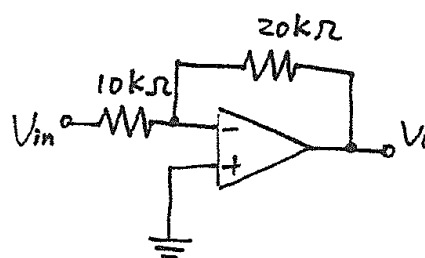


Figure 2

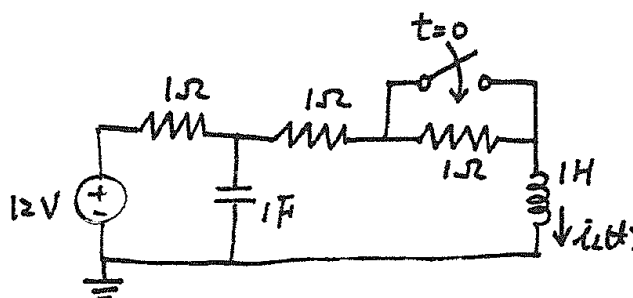


Figure 3

試題隨卷繳回