

1. (15%) Please analyze the operational circuit shown as Figure 1. Find the output current i_{out} as a function of v_{in} .

 


Figure 1

 


Figure 2

2. (20%) Please analyze the BJT circuit shown in Figure 2. The circuit parameters can be given as $V_{CC} = 20\text{ V}$; $R_B = 200\text{ k}\Omega$; $R_{C1} = 10\text{ k}\Omega$; $R_{E1} = 1\text{ k}\Omega$; $R_{E2} = 8\text{ k}\Omega$ and $\beta = 50$

- (a) (10%) Please find the DC biased current at the collector of Q_1 and Q_2 .
 (b) (10%) Please find the small-signal gain of v_o/v_i .

3. (15%) Please analyze the MOSFET circuit shown as Figure 3. Assume all circuit are properly biased and operated in saturation region. Assume the transconductance of NMOS is $g_{m,N}$ and the transconductance of PMOS is $g_{m,P}$. And there is the same finite output resistance (r_o) of these MOSFETs.

- (a) (3%) Please write down the topology of the MOSFET amplifier of each circuit
 (b) (4%) Please derive the small-signal gain of Fig. 3(a)
 (c) (4%) Please derive the small-signal gain of Fig. 3(b)
 (d) (4%) Please derive the small-signal gain of Fig. 3(c)

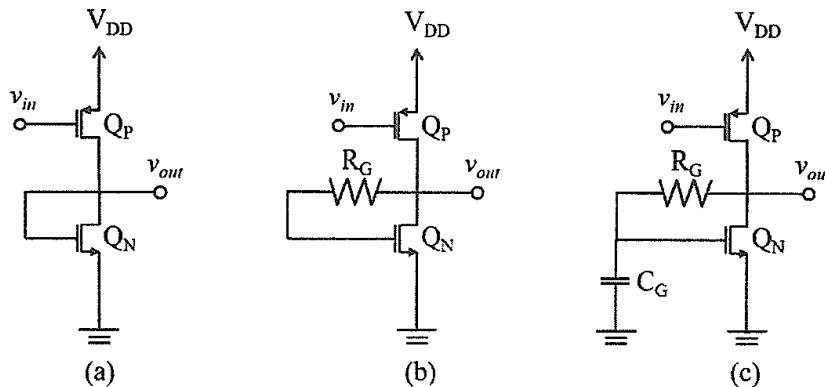


Figure 3

見背面

4. (15%) For a static four-input NAND gate with $L = 0.18 \mu\text{m}$, all transistor sizes are chosen to match the delay of a basic CMOS inverter with $(W/L)_n = n$ and $(W/L)_p = p$.
- (5%) Please sketch the CMOS circuit for a static four-input NAND gate.
 - (6%) For a static four-input NAND gate with $n = 1.5$ and $p = 3$, please give the sizes (W/L) of all transistors.
 - (4%) For the static four-input NAND gate, find the ratio of the maximum to minimum current available to (a) charge a load capacitance and (b) discharge a load capacitance.
5. (25%) Design the circuit in Figure 4 to obtain a dc voltage of $+0.1 \text{ V}$ at each of the drains of Q_1 and Q_2 when $v_{G1} = v_{G2} = 0 \text{ V}$. Operate all transistors at $V_{OV} = 0.15 \text{ V}$ and assume that for the process technology in which the circuit is fabricated, $V_{tn} = 0.4 \text{ V}$ and $\mu_n C_{ox} = 400 \mu\text{A}/\text{V}^2$. Neglect channel-length modulation.
- (4%) Determine the value of R_D .
 - (12%) Determine the W/L ratios of Q_1 , Q_2 , Q_3 , and Q_4 .
 - (4%) Determine the value of R .
 - (5%) What are the lower and upper limits of the input common-mode voltages?

 


Figure 4

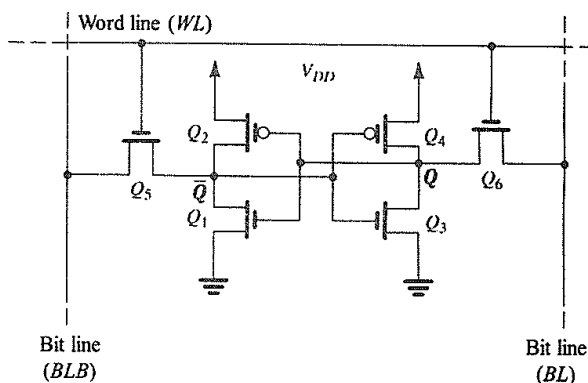


Figure 5

6. (10%) Before the read operation, both bit lines (BL and BLB) are precharged to V_{DD} . Find the maximum allowable $(W/L)_a$ for the access transistors of the SRAM cell shown in Figure 5 so that in a read operation, the voltages at Q and \bar{Q} do not change by more than a threshold voltage $|V_t|$. Assume that the SRAM is fabricated in a $0.18 \mu\text{m}$ technology for which $V_{DD} = 1.8 \text{ V}$, $V_{tn} = |V_{tp}| = 0.5 \text{ V}$ and that $(W/L)_n = 1.5$ for pull-down devices.

試題隨卷繳回