

1. Choose ALL correct statements from the following. [5%]
 - (a) For a common-base amplifier, the magnitude of the voltage gain is always less than unity.
 - (b) A common-base amplifier typically has a low input resistance.
 - (c) A common-collector amplifier typically has a high output resistance.
 - (d) The intrinsic gain of a common-emitter amplifier does not strongly depend on the bias current.
 - (e) The input resistance of a common-emitter amplifier does not change with the degeneration resistance.
2. Choose ALL correct statements from the following. [5%]
 - (a) The low-frequency response of an amplifier is due to parasitic capacitances of the transistors.
 - (b) The parasitic capacitance of an amplifier can be neglected at higher frequencies.
 - (c) The high-frequency response of an amplifier does not change significantly with the coupling capacitors.
 - (d) The influence of coupling and parasitic capacitances can be neglected at mid-band frequencies.
 - (e) Trade-off typically exists between amplifier gain and bandwidth.
3. Choose ALL correct statements from the following. [5%]
 - (a) Complementary CMOS logic has zero dynamic power dissipation.
 - (b) Complementary CMOS logic has zero static power dissipation.
 - (c) The delay of complementary CMOS logic can be significantly reduced by increasing the transistor size.
 - (d) The noise margin of a CMOS inverter can be adjusted by the aspect ratios of the transistors.
 - (e) The dynamic power of complementary CMOS logic is independent of the supply voltage.
4. Choose ALL correct statements from the following. [5%]
 - (a) For an op-amp circuit with a negative feedback, the output voltage is finite.
 - (b) Virtual-short property always applies for an op-amp circuit with a negative feedback.
 - (c) Negative feedback is widely used for bi-stable circuit applications.
 - (d) An op-amp inverting amplifier has very high input resistance.
 - (e) Positive feedback is used in an op-amp non-inverting amplifier.
5. The circuit in Fig. 5 is a second-order filter
 - (a) Derive the transfer function of the filter. [10%]
 - (b) If gain peaking is not wanted, how do you choose the value of Q ? [10%]
 - (c) Find the magnitude and phase of the filter gain at $\omega = 1/(RC)$. [10%]

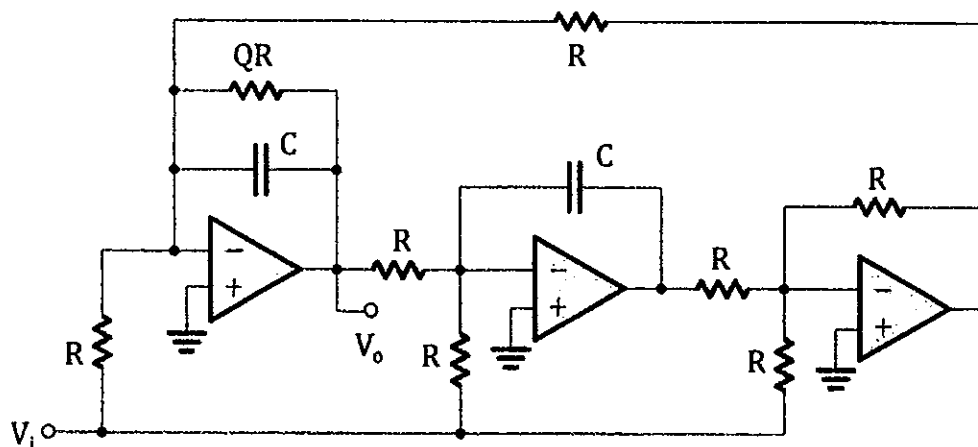


Fig. 5

見背面

6. For the cascode amplifiers in Fig. 6, the MOSFET parameters are given as $\mu_n C_{ox} = 400 \mu\text{A}/\text{V}^2$, $V_t = 0.5 \text{ V}$, $V_A' = 5 \text{ V}/\mu\text{m}$, $W = 3.6 \mu\text{m}$ and $L = 0.36 \mu\text{m}$, while the BJT parameters are given as $\beta = 100$ and $V_A = 10 \text{ V}$.
- Consider the circuit in Fig. 6(a). For $I = 180 \mu\text{A}$, find the minimum acceptable value of the dc voltage V_{BIAS} . What is the minimum value of the output swing? [10%]
 - For $I = 180 \mu\text{A}$, $V_{\text{BIAS}} = 1.2 \text{ V}$ and $V_{\text{DD}} = 1.8 \text{ V}$, find the voltage gain (v_o/v_i) and output resistance (R_{out}) of the amplifier in Fig. 6(a). [10%]
 - For $I = 80 \mu\text{A}$, $V_{\text{BIAS}} = 1.2 \text{ V}$ and $V_{\text{DD}} = 1.8 \text{ V}$, find the voltage gain (v_o/v_i) and output resistance (R_{out}) of the amplifier in Fig. 6(b). [10%]
 - If a voltage gain of -7200 is required for the amplifier in Fig. 6(a), how do you choose the value of I ? [10%]
 - Assume that the voltage gain in Fig. 6(a) is A_{v1} and the voltage gain in Fig. 6(b) is A_{v2} . How does the ratio of A_{v1}/A_{v2} depend on the bias current I ? [10%]

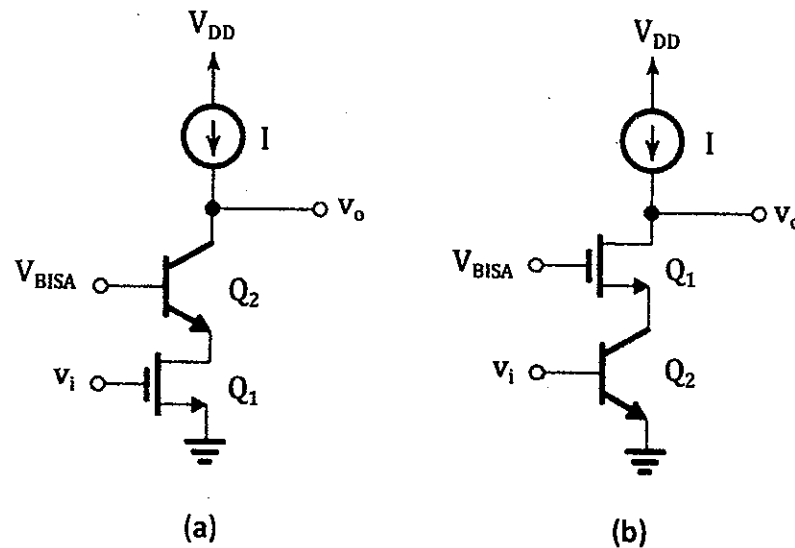


Fig. 6