
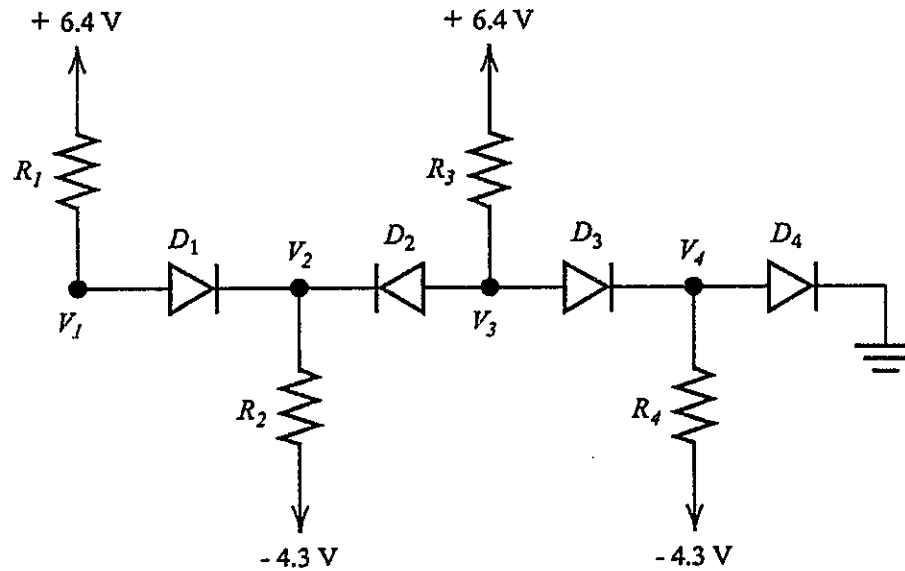


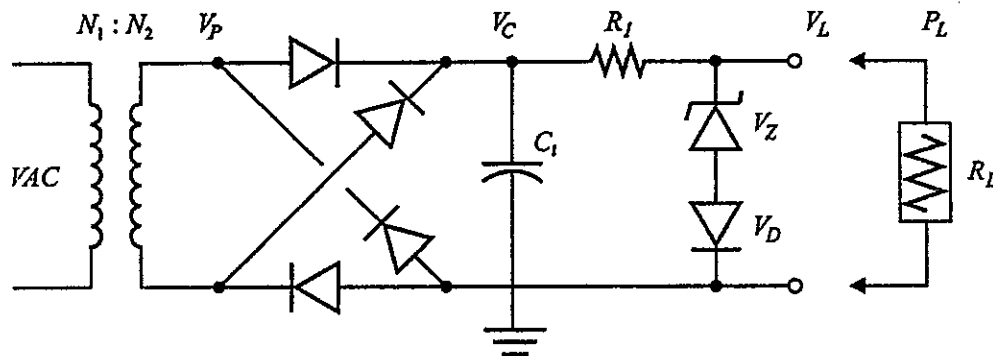
1. (20%) Determine node voltages V_1, V_2, V_3, V_4 and the currents through each of the diodes for $R_1 = 4.0 \text{ k}\Omega, R_2 = R_3 = 2.5 \text{ k}\Omega$ and $R_4 = 5.0 \text{ k}\Omega$. Assume all the diodes follow common voltage drop (CVD) model.



2. (15%) For the full-wave rectifier (FWR) topology shown in the figure, please choose component values that will support a Zener diode regulated 240 mW, 6V application from a 120 V, 60 Hz power tap. Transformer turns ratio $N_{12} = 12:1$. Assume all diodes are Si power diodes ($V_D = 0.8 \text{ V}$).
- Determine V_C and V_P .
 - If $V_C(\text{min}) = 8.0 \text{ V}$ with the load connected, what values of R_1 and C_1 are required, assuming that the current through the Zener diode approaches zero when V_C approaches $V_C(\text{min})$.
 - What average power must the Zener diode dissipate when the load is not connected?




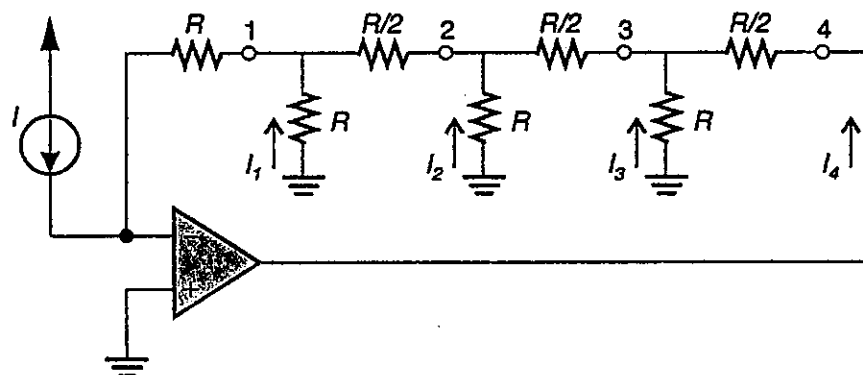3. (20%) The circuit is shown in the figure. Assume the OP amplifier is ideal. Please answer the questions in terms of the resistance R and the input current I .
- Find the resistances looking into node 1, R_1 ; node 2, R_2 ; node 3, R_3 ; and node 4, R_4 .
 - Find the currents I_1, I_2, I_3 , and I_4 .
 - Find the voltages at nodes 1, 2, 3, and 4, that is, V_1, V_2, V_3 , and V_4 .




見背面

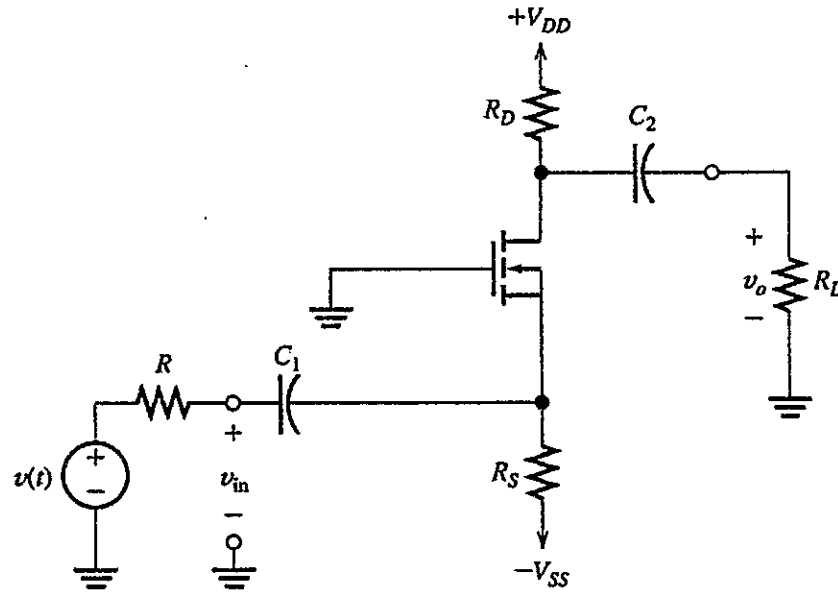4. (20%) Consider the common-gate amplifier shown in the figure. The MOSFET has $K = 1.5 \text{ mA/V}^2$ and $V_{t0} = 1\text{V}$, $r_d = \infty$. The supply voltages are $V_{DD} = 15 \text{ V}$ and $V_{SS} = 15 \text{ V}$. The resistances are $R_S = 3 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, and $R_D = 3 \text{ k}\Omega$. Determine the Q point and the transconductance of the device, g_m . Determine the input resistance and the voltage gain.



5. (25%) Consider the common-emitter amplifier of the figure.

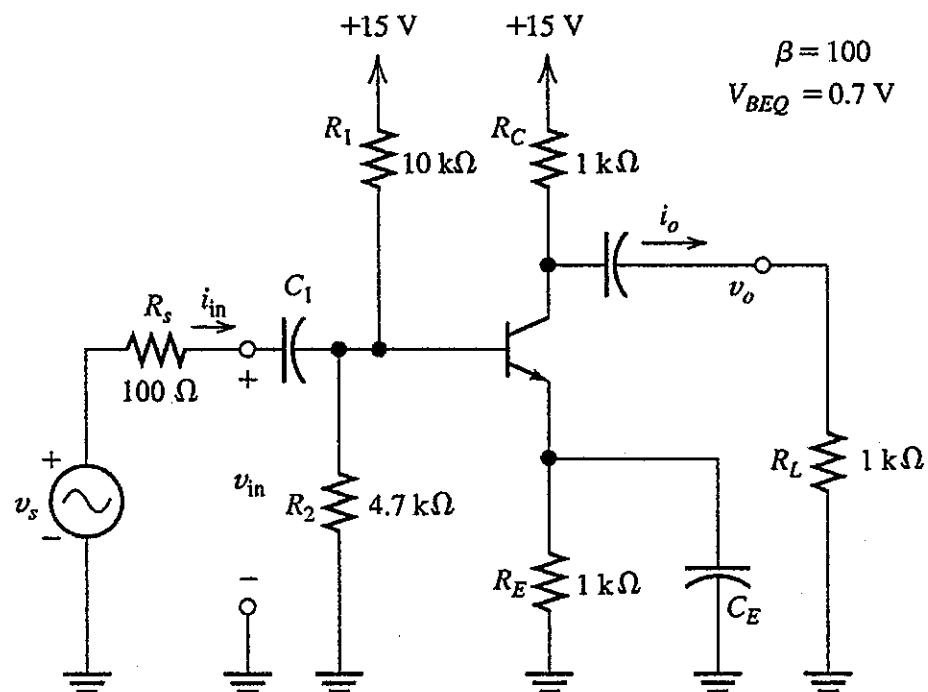- (a) Draw the dc circuit and find I_{CQ} . Find the resistance, r_{π} , in the small-signal equivalent circuit. Then calculate values for voltage gain A_v , the voltage gain in an open circuit A_{vo} , input impedance Z_{in} , the current gain A_i , the power gain G , and output impedance Z_o . Assume that the circuit is operating in the midband region for which the coupling and the bypass capacitors are short circuits.
- (b) Repeat (a) if all resistance values, including R_S and R_L , are increased in value by a factor of 100. Prepare a table comparing the results for the low-impedance amplifier with those for the high-impedance amplifier.



試題隨卷繳回