
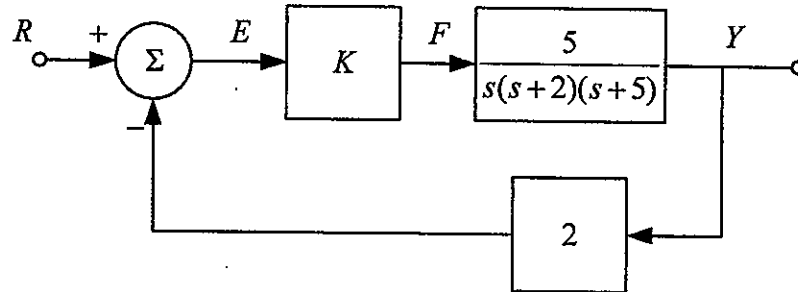


Problem I (40%). For the system shown below, sketch the Nyquist plot and apply the Nyquist criterion to

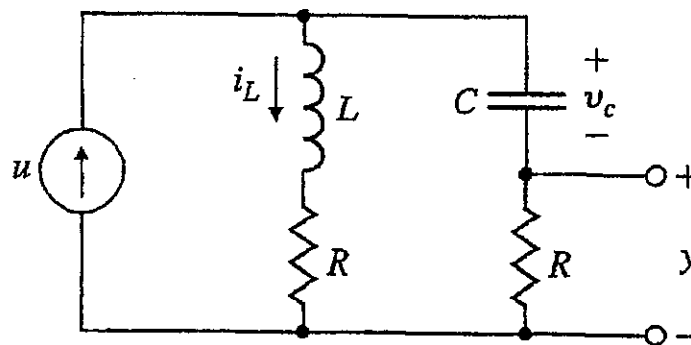- (a) (20%) Determine the range of values of K (both positive and negative) for which the system will be stable, and
- (b) (20%) Determine the number of roots in the right-half-plane for those values of K for which the system is unstable. Check your answer using a rough root-locus sketch.



Problem II (60%). Consider the electric circuit shown below



- (a) (20%) Derive the internal state equations for the circuit. The input u is a current, and the output y is a voltage. Let $x_1 = i_L$ and $x_2 = v_c$.
- (b) (20%) What condition(s) on R , L , and C will guarantee that the system is controllable?
- (c) (20%) Find the system transfer function using matrix algebra.