

1. (15%) Consider the amplifier of Fig. 1 with a common-mode input voltage of +5 V (dc) and a differential input signal of 10-mV-peak sine wave. Let $(2R_1) = 1 \text{ k}\Omega$, $R_2 = 0.5 \text{ M}\Omega$, and $R_3 = R_4 = 10 \text{ k}\Omega$. Please find the output voltage (v_o).

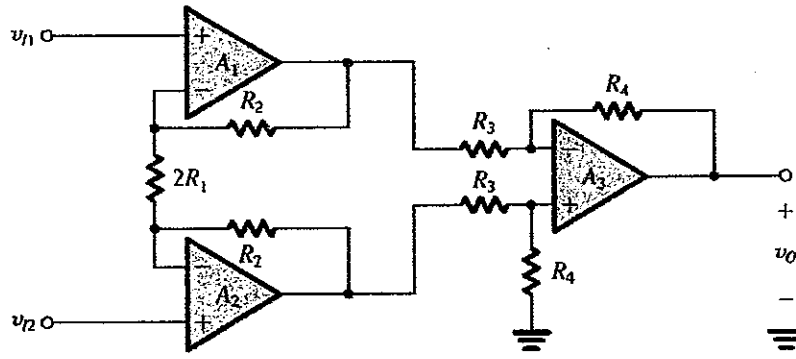


Fig. 1.

2. (20%) The 6.8-V zener diode in the circuit of Fig. 2 is specified to have $V_Z = 6.8 \text{ V}$ at $I_Z = 5 \text{ mA}$, $r_z = 20 \Omega$, and $I_{ZK} = 0.2 \text{ mA}$. The supply voltage V^+ is nominally 10 V but can vary by $\pm 1 \text{ V}$. (a) Find V_o with no load and with V^+ at its nominal value. (b) Please find the change in V_o when $R_L = 2 \text{ k}\Omega$ and $R_L = 0.5 \text{ k}\Omega$. (c) What is the minimum value of R_L for which the diode still operates in the breakdown region?

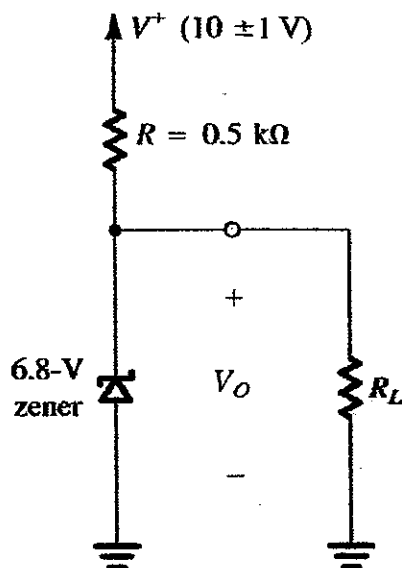


Fig. 2.

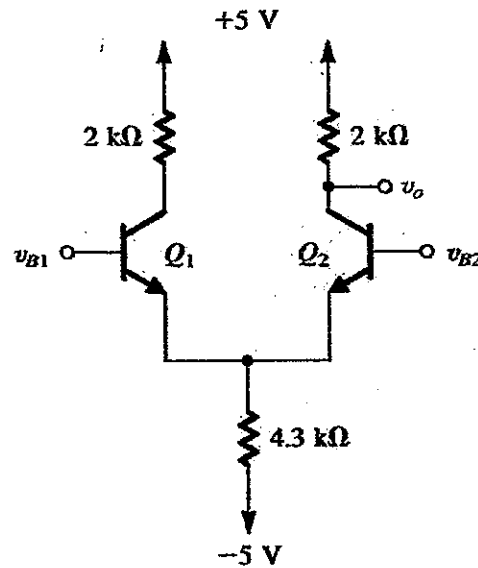


Fig. 3.

3. (15%) The differential amplifier circuit of Fig. 3 utilizes a resistor connected to the negative power supply to establish the bias current I . $V_{BE} = 0.7 \text{ V}$.
- (a) For $v_{B1} = v_{id}/2$ and $v_{B2} = -v_{id}/2$, where v_{id} is a small signal with zero average, please find the magnitude of the differential gain, $|v_o/v_{id}|$.
- (b) For $v_{B1} = v_{B2} = v_{icm}$, where v_{icm} has a zero average, find the magnitude of the please common-mode gain, $|v_o/v_{icm}|$.
- (c) Please calculate the CMRR.

4. (20%) The variable resistor in the circuit in Fig. 4 is adjusted for maximum power transfer to R_o . (a) Find the value of R_o . (b) Find the maximum power that can be delivered to R_o .

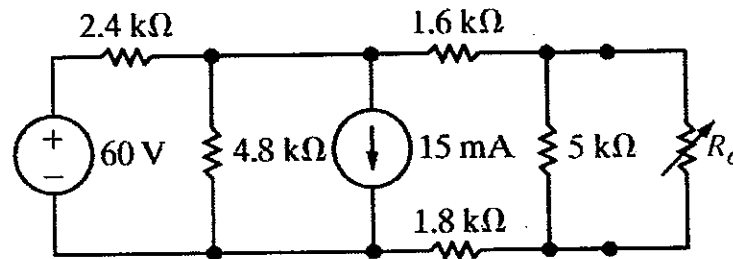


Fig. 4.

5. (20%) The switch in the circuit in Fig. 5 has been in position 1 for a long time. At the $t = 0$, switch moves instantaneously to position 2. (a) Find $v_o(t)$ for $t \geq 0^+$. (b) What percentage of the initial energy stored in the inductor is eventually dissipated in the 6Ω resistor?

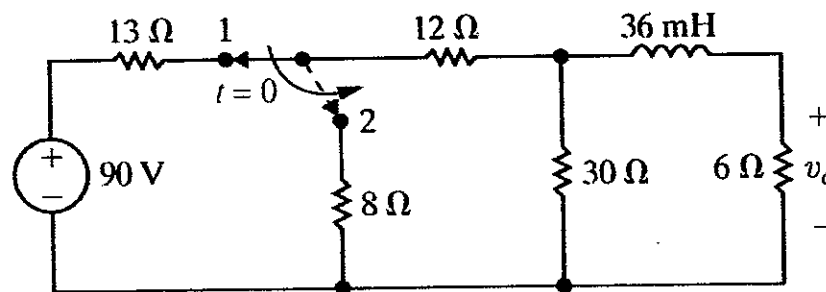


Fig. 5.

6. (10%) Please construct the Bode plots (magnitude and phase) for the transfer function.

$$H(\omega) = \frac{200j\omega}{(j\omega + 2)(j\omega + 10)}$$